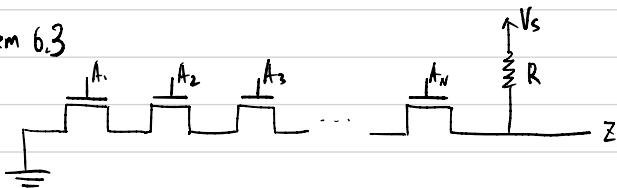


EEC HW3 2021-16988 Jaewan Park.

Problem 6.3



$$\text{NAND } (A_1 \sim A_N) = 1 \Rightarrow V_z = V_s$$

$$\text{NAND } (A_1 \sim A_N) = 0 \Rightarrow V_z = V_s \times \frac{NR_{ON}}{R + NR_{ON}} = V_s \times \frac{N}{100 + N}$$

V_z when $Z=0$ should satisfy $V_z \leq V_{OL}$


$$\therefore V_s \times \frac{N}{100 + N} \leq 1 \quad N \leq \frac{100}{V_s - 1}$$

When all $A_1 = \dots = A_N$ are on, we have maximum P.

$$\therefore P_{max} \geq \frac{V_s^2}{\sum R} = \frac{V_s^2}{NR_{ON} + R} = \frac{V_s^2}{(N+100)k}$$

$$\therefore \text{Maximum } N = \frac{100}{V_s - 1}, \text{ Maximum Power} = \frac{V_s^2}{(N+100)k} = \frac{V_s(V_s-1)}{100k}$$

Problem 6.6 (b)

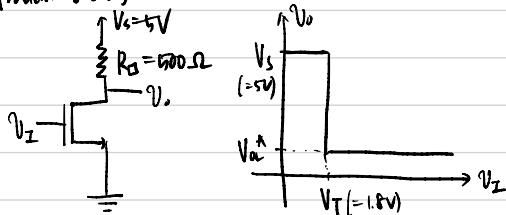

$$V_{OL}^* = V_s \times \frac{R_{ON}}{R_{ON} + R} = 5 \times \frac{\frac{L}{W}}{\frac{L}{W} + 500 \frac{L}{W}} \leq 0.5.$$

$$\therefore \frac{L}{W_R} \geq 18 \cdot \frac{L}{W}$$

Since the total area is $L \cdot W + L_R \cdot W_R$,

we have minimum area when $L = W_R = 0.5 \mu m$. Then $L_R = W = \frac{3}{15} \mu m$.

$$\therefore \text{Minimum Area} = \frac{3}{15} \mu m^2$$

When the MOSFET is on, we have maximum power.

$$\therefore P_{max} = \frac{V_s^2}{IR} = \frac{V_s^2}{R_{ON} + R}$$

Exercise 1.10

$$(a) V_o = V_s - R_L \cdot i_C = V_s - R_L \cdot \beta \cdot i_B$$

$$= V_s - R_L \cdot \beta \cdot \frac{V_2 - 0.6}{R_2}$$

$$= 5 - 10 \cdot 100 \cdot \frac{V_2 - 0.6}{500}$$

$$= 6.2 - 2V_2$$

(b) For the BJT to remain in the active region, i_B should be nonnegative.

Then we have

$$i_B = \frac{V_2 - 0.6}{R_2} \geq 0, \quad V_2 \geq 0.6$$

Therefore the minimum value of V_2 is 0.6V

then $i_B = 0, i_C = \beta i_B = 0,$

$$V_o = 6.2 - 2V_2 = 5 \text{ V}$$

Problem 1.2

$$(a) i) V_{GS} (= V_{ZN}) < V_T$$

$$V_{out} = V_s \quad (\because \text{open switch})$$

$$ii) V_{GS} (= V_{ZN}) \geq V_T$$

At first, when V_{IN} is not sufficiently large, the MOSFET enters a saturation region.

$$\text{Then } V_{out} = V_s - R I_{DS} = V_s - R \cdot \frac{k}{2} (V_{GS} - V_T)^2 = V_s - \frac{kR}{2} (V_{ZN} - V_T)^2$$

If V_{IN} gets sufficiently large, the MOSFET acts as a closed switch, so no current flows through R .

$$\text{Then } V_{out} = 0$$

Let the value of V_{IN} between the saturation and closed switch regions V_{INT}

$$\therefore V_{out} = \begin{cases} V_s & (0 \leq V_{ZN} < V_T) \\ V_s - \frac{kR}{2} (V_{ZN} - V_T)^2 & (V_T \leq V_{ZN} < V_{INT}) \\ 0 & (V_{ZN} \geq V_{INT}) \end{cases}$$

(c) At $V_{IN} = V_{IN_T}$, we should have $V_{out} = V_s - R_i \cdot i_{DS} = 0$, so $i_{DS} = \frac{V_s}{R}$.


$$\therefore i_{DS} = \frac{V_s}{R} = \frac{k}{2} (V_{IN_T} - V_T)^2$$

$$V_{IN_T} = \sqrt{\frac{2V_s}{kR}} + V_T$$

Substituting the given values gives $V_{IN_T} = 2V$

$$\begin{cases} V_s = 15V & (0 \leq V_{IN} < 1) \\ V_s - \frac{kR}{2} (V_{IN} - V_T)^2 = 15 - 15(V_{IN} - 1)^2 & (1 \leq V_{IN} < 2) \\ 0 & (2 \leq V_{IN} \leq 3) \end{cases}$$

Problem 1.14

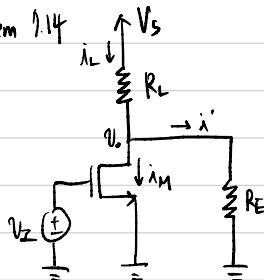

It is given that the MOSFET operates in saturation.

Then we obtain

$$V_o = R_E i'$$

$$V_s - R_L i_L = V_o$$


$$i_M = \frac{k}{2} (V_z - V_T)^2 \quad (\because \text{saturation})$$

$$\text{Since } i_L = i' + i_M \quad (\because \text{KCL})$$

$$\frac{V_s - V_o}{R_L} = \frac{V_o}{R_E} + \frac{k}{2} (V_z - V_T)^2$$

$$\therefore V_o = \frac{2V_s R_E - k R_E R_L (V_z - V_T)^2}{2(R_L + R_E)}$$

Problem 1.11

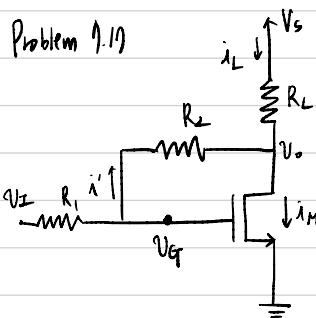

It is given that the MOSFET operates in saturation.

$$V_G = \frac{R_g}{R_1 + R_2} V_z + \frac{R_1}{R_1 + R_2} V_o \quad (\because \text{superposition})$$

$$V_s - R_L i_L = V_o$$

$$V_G - R_2 i' = V_o$$

$$i_M = \frac{k}{2} (V_G - V_T)^2 \quad (\because \text{saturation})$$


$$\text{Since } i_L + i' = i_M \quad (\because \text{KCL}),$$

$$\frac{V_s - V_o}{R_L} + \frac{V_G - V_o}{R_2} = \frac{k}{2} (V_G - V_T)^2 \Rightarrow \frac{V_s - V_o}{R_L} + \frac{V_z - V_o}{R_1 + R_2} = \frac{k}{2} (V_G - V_T)^2$$

V_o is the root of the above equation (quadratic equation on V_o , solvable)

2019 2nd exam #1

(a).

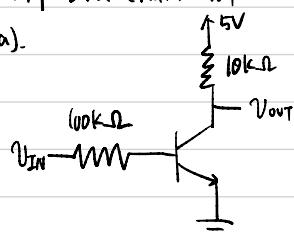

i) $V_{in} \leq V_{DN} = 0.7V$: cut-off

$$V_{out} \approx V_S = 5V$$

ii) $V_{DN} \leq V_{2N} \leq V_{2N}$: active


$$V_{out} = V_S - R_L \cdot \beta \cdot \frac{V_{2N} - V_{DN}}{R_2}$$

$$= 12 - 10 V_{in}$$

V_{IN_T} is the voltage where $V_{out} = V_{sat}$ ($= 0.2V$). so $V_{IN_T} = 1.18V$

iii) $V_{2N} \geq V_{2NT}$: saturation


$$V_{out} = V_{sat} = 0.2V$$

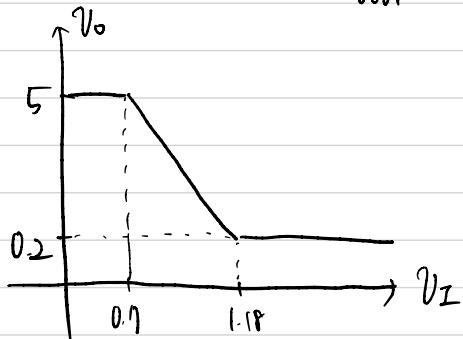

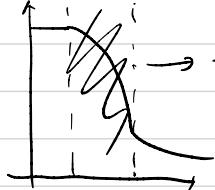(b) When active,

$$\frac{dV_o}{dV_i} = -10 \Rightarrow \text{Voltage Gain}$$

In the case of MOSFET, the gain is small since



→ this region is non-linear, so BJT amplifiers have rather better voltage gain.