

EXERCISE 12.2 For each of the circuits in Figure 12.66, find and sketch the indicated zero-input response corresponding to the indicated initial conditions

- a) In Figure 12.66, find v_2 , assuming $v_1(0) = 1 \text{ V}$, $v_2(0) = 0$

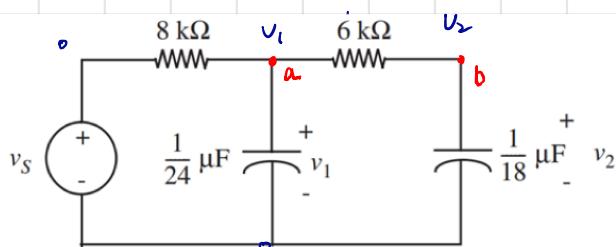


FIGURE 12.66

① KCL at a.

$$\frac{V_1}{8} + \frac{V_1 - V_2}{6} + \frac{1}{24} \frac{dV_1}{dt} = 0 \Rightarrow 7V_1 - 4V_2 + \frac{dV_1}{dt} = 0 \dots (1)$$

② KCL at b.

$$\frac{V_1 - V_2}{6} = \frac{1}{18} \frac{dV_2}{dt} \Rightarrow V_1 = V_2 + \frac{1}{3} \frac{dV_2}{dt} \dots (2)$$

from ① & ② $\frac{d^2V_2}{dt^2} + 10 \frac{dV_2}{dt} + 9V_2 = 0$

$$V_2(t) = A_1 e^{-9t} + A_2 e^{-t} \dots (3)$$


$$V_2(0) = A_1 + A_2 = 0 \dots (4)$$

from ② & ③ $V_1(t) = A_1 e^{-9t} + A_2 e^{-t} + \frac{1}{3}(-9A_1 e^{-9t} - A_2 e^{-t})$


$$V_1(0) = A_1 + A_2 - \frac{1}{3}A_2 = 1 \Rightarrow -6A_1 + 2A_2 = 3 \dots (5)$$

from ④ & ⑤ $A_1 = -\frac{3}{8}$ $A_2 = \frac{3}{8}$
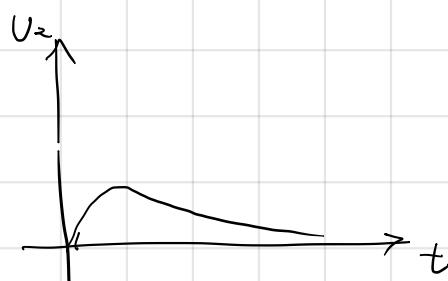
$$\therefore V_2(t) = -\frac{3}{8} e^{-9t} + \frac{3}{8} e^{-t} = \frac{3}{8} e^{-t} (1 - e^{-8t})$$



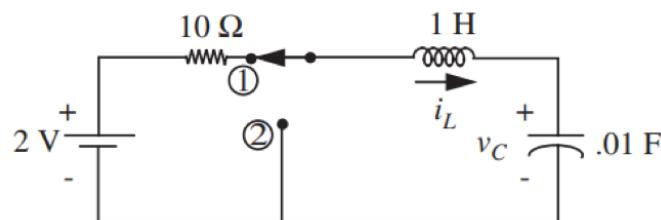PROBLEM 12.6 In the circuit in Figure 12.77, the switch has been in position 1 for all $t < 0$. At $t = 0$, the switch is moved to position 2 (and remains there for $t > 0$). Find and sketch $v_C(t)$ and $i_L(t)$ for $t > 0$.



$$V_c(0^-) = V_c(0^+) = 2, \quad i_L(0^-) = i_L(0^+) = 0$$

$$\text{when } t > 0, \quad i_L = C \frac{dv_C}{dt} \quad \dots \quad (1)$$

$$v_C + L \frac{di_L}{dt} = 0 \quad \dots \quad (2)$$

$$\text{from } (1) \text{ & } (2) \quad i_L = -LC \frac{d^2 v_C}{dt^2} \Rightarrow \frac{d^2 i_L}{dt^2} + \frac{1}{LC} i_L = 0 \Rightarrow \frac{d^2 i_L}{dt^2} + 100 i_L = 0.$$

$$i_L = A_1 e^{10jt} + A_2 e^{-10jt} \quad \dots \quad (3)$$

$$i_L(0^+) = A_1 + A_2 = 0 \quad \dots \quad (4)$$



$$\text{from } (2) \text{ & } (3) \quad v_C = - (10jA_1 e^{10jt} - 10jA_2 e^{-10jt})$$

$$v_C(0^+) = -10jA_1 + 10jA_2 = 2 \quad \Rightarrow \quad A_1 - A_2 = -0.2j$$

$$\text{from } (4) \text{ & } (5) \quad A_1 = -0.1j \quad A_2 = 0.1j$$

$$\therefore v_C(t) = e^{10jt} + e^{-10jt} = 2\cos 10t$$

$$\therefore i_L(t) = C \frac{dv_C}{dt} = 0.01 \times (-2 \times 10 \times \sin 10t) = -0.2 \sin 10t$$

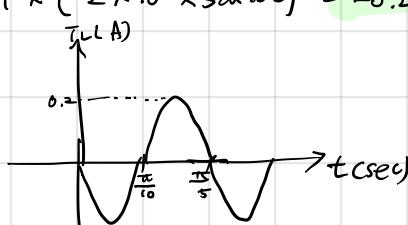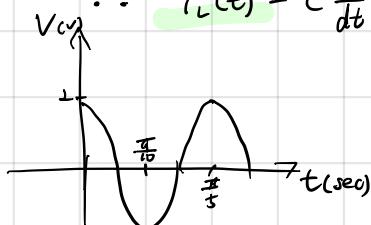

EXERCISE 13.13 In the network shown in Figure 13.72,

$$R = 1 \text{ k}\Omega \quad C_1 = 20 \mu\text{F} \quad C_2 = 20 \mu\text{F}$$

- Determine the magnitude and phase of $H(j\omega)$, the transfer function relating V_0/V_i .
- Given $v_i(t) = \cos(100t) + \cos(10000t)$, determine the sinusoidal steady state output voltage, $v_o(t)$.


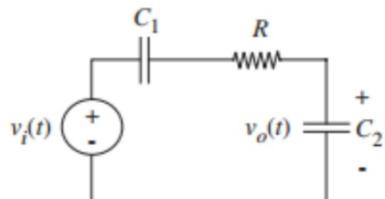


FIGURE 13.72

(a) Determine the magnitude and phase of $H(j\omega)$, the transfer function relating V_0/V_i .

The impedance circuit is as follows:

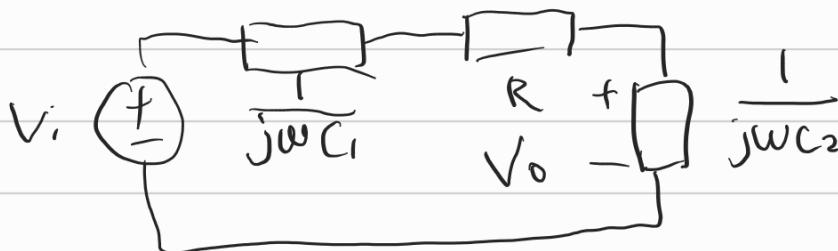

By the impedance method,

$$\frac{V_o}{V_i} = \frac{\frac{1}{j\omega C_2}}{R + \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}} = \frac{\frac{1}{20\mu\text{F}j\omega}}{1k + \frac{1}{20\mu\text{F}j\omega} + \frac{1}{20\mu\text{F}j\omega}}$$

$$= \frac{\frac{1}{2 + \frac{j\omega}{50}}}{\frac{1}{2} \times \frac{1 + \frac{j\omega}{100}}{1 + \frac{j\omega}{100}}}$$

$$\text{Magnitude: } \left| \frac{V_o}{V_i} \right| = \frac{1}{2 \sqrt{1 + \frac{\omega^2}{100^2}}}$$

$$\text{Phase: } \angle \left[\frac{V_o}{V_i} \right] = \phi = \tan^{-1} \left(-\frac{\omega}{100} \right)$$

(b) Given $V_{in}(t) = \cos(100t) + \cos(10000t)$, determine the sinusoidal steady state output voltage, $V_o(t)$

From the conclusion of (a), we get

$$V_o(t) = \frac{1}{2\sqrt{1+\frac{\omega^2}{r^2}}} \cos(\omega t + \phi), \text{ where } \tan \phi = -\frac{\omega}{r}$$

By the superposition principle, we can calculate the contributions of $\cos(100t)$ and $\cos(10000t)$ separately

$$\textcircled{1} \quad \cos(100t) \rightarrow \omega = 100$$

$$\tan \phi = -1 \Rightarrow \phi = -\frac{\pi}{4}$$

$$V_{o1}(t) = \frac{1}{2\sqrt{2}} \cos(100t - \frac{\pi}{4})$$

$$\textcircled{2} \quad \cos(10000t) \rightarrow \omega = 10000$$

$$\tan \phi = -100$$

$$V_{o2}(t) = \frac{1}{2\sqrt{10001}} \cos(10000t - \tan^{-1}(-100))$$

By \textcircled{1} & \textcircled{2},

$$V_o(t) = \frac{1}{2\sqrt{2}} \cos(100t - \frac{\pi}{4}) + \frac{1}{2\sqrt{10001}} \cos(10000t - \tan^{-1}(-100))$$

PROBLEM 13.4 Refer to Figure 13.80 for this problem. Assume $R_1 = 1 \text{ k}\Omega$ and $L_1 = 10 \text{ mH}$.

- Find the transfer function $H(j\omega) = V_1/V_o$.
- Find R so that the DC gain is $1/10$.
- Find a value of L so that the response at high frequencies is equal to response at DC.

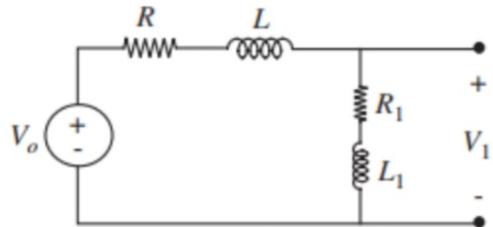


FIGURE 13.80

(a) Find the transfer function $H(j\omega) = V_1/V_o$

$$\frac{V_1}{V_o} = \frac{R_1 + j\omega L_1}{R + j\omega L + R_1 + j\omega L_1}$$

(b) Find R so that the DC gain is $1/10$

We can get the DC gain by substituting ω with $\omega=0$

$$\text{DC gain} = \frac{R_1}{R+R_1} = \frac{1}{R+1} = \frac{1}{10}$$

$$\Rightarrow R = 9 \text{ k}\Omega$$

(c) Find a value of L so that the response at high frequencies is equal to response at DC

High frequencies: $\omega \rightarrow \infty$

Note that as $\omega \rightarrow \infty$, $L_1/L_o \rightarrow \frac{L_1}{L+L_1} = \frac{f_0}{L+f_0}$

$$\frac{10}{L+f_0} = \frac{1}{10} \quad \Rightarrow \quad L = 90 \text{ mH}$$

EXERCISE 15.12 Find and label clearly the Thévenin equivalent for the network in Figure 15.53.

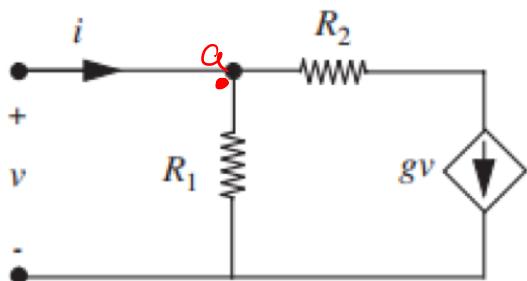


FIGURE 15.53

To get V_{th} , assume $i = 0$.

$$\text{then } R_1 g V_{th} = V_{th}$$

In order to satisfy the equation regardless R_1 and g , V_{th} should be zero.

$$\therefore V_{th} = 0$$

To get R_{th}

$$\text{apply KCL at } a, \text{ then } i = gV + \frac{v}{R_1} = V(g + \frac{1}{R_1})$$

$$\therefore R_{th} = \frac{v}{i} = \frac{v}{V(g + \frac{1}{R_1})} = \frac{R_1}{1 + R_1 g}$$

Exercise 15.13 Find i in terms of v for the linear network in Figure 15.18. Assume an idealized operational amplifier.

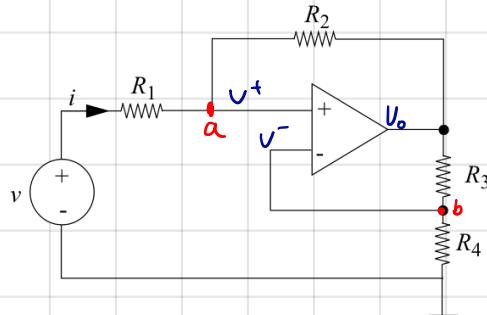


Figure 15.18:

$$i = \frac{v - V^+}{R_1}, \text{ we need to find } V^+$$

- KCL at 'a', $\frac{V - V^+}{R_1} = \frac{V^+ - V_o}{R_2} \dots \textcircled{1}$

- at 'b', $V^- = \frac{R_4}{R_3 + R_4} V_o$

Because $V^+ = V^-$ at an idealized Op Amp, $V^+ = \frac{R_4}{R_3 + R_4} V_o$
 $\Rightarrow \frac{R_3 + R_4}{R_4} V^+ = V^o \dots \textcircled{2}$

from $\textcircled{1} \& \textcircled{2}$, $V^+ = \left(\frac{R_2 R_4}{R_2 R_4 + R_1 R_3} \right) \cdot v$

$$\therefore i = \frac{V - V^+}{R_1} = \frac{v}{R_1} \left(\frac{-R_3 - R_2 R_4}{R_2 R_4 + R_1 R_3} \right) = \frac{-R_3}{R_2 R_4 + R_1 R_3} \cdot v = \frac{R_3}{R_1 R_3 - R_2 R_4} \cdot v$$

EXERCISE 15.24 An operational amplifier is connected as shown in Figure 15.65.

- What is the gain of the amplifier for $\omega = 0$?
- Find the expression for $V_o(j\omega)/V_i(j\omega)$.

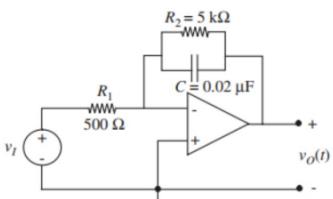


FIGURE 15.65

$$\frac{V_I}{R_1} = - \frac{V_O}{R_2} - \frac{V_O}{\frac{1}{j\omega C}} = - \left(\frac{1}{R_2} + j\omega C \right) V_O$$

$$\begin{aligned} \therefore \frac{V_O}{V_I} &= - \frac{1}{R_1} \cdot \frac{1}{\frac{1}{R_2} + j\omega C} \\ &= - \frac{1}{R_1} \cdot \frac{R_2}{1 + j\omega C R_2} \end{aligned}$$

$$(a) \omega = 0, \text{ gain} = \frac{V_O}{V_I} = - \frac{R_2}{R_1} = \frac{-5 \cdot 10^3}{5 \cdot 10^2} = \boxed{-10}$$

$$\begin{aligned} (b) \frac{V_O(j\omega)}{V_I(j\omega)} &= - \frac{1}{R_1} \cdot \frac{R_2}{1 + j\omega C R_2} \\ &= \boxed{- \frac{10}{1 + j\omega \cdot 0.1}} \end{aligned}$$

{ unit: R_1, R_2 ($k\Omega$)
 C (μF)
 ω ($rad/msec$)

PROBLEM 15.34 The circuit shown in Figure 15.105 behaves like an RLC circuit.

- a) Find the transfer function V_4/V_1 . (You may assume that the Op Amp is ideal, that is $V^+ = V^-$ to simplify your calculations.)

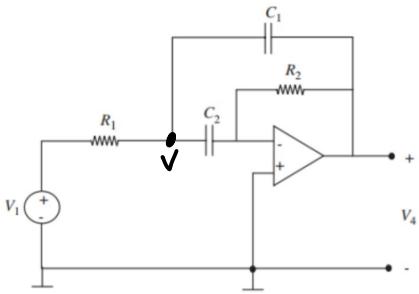


FIGURE 15.105

- c) This circuit is known as an RC active filter. Is it a low-pass, high-pass, or band-pass filter? What is the expression for bandwidth in terms at R_1, C_1 , etc.? That is, $B = \omega_2 - \omega_1$ where ω_1 and ω_2 are the half power frequencies.

$$\textcircled{1} \quad \frac{V_1 - V}{R_1} = \frac{V - V_4}{j\omega C_1} + \frac{V}{j\omega C_2}$$

$$\Rightarrow \frac{V_1 - V}{R_1} = (j\omega C_1 + j\omega C_2)V - j\omega C_1 V_4$$

$$\Rightarrow V_1 = (j\omega R_1 C_1 + j\omega R_1 C_2 + 1)V - j\omega R_1 C_1 V_4$$

$$\textcircled{2} \quad \frac{V}{j\omega C_2} = -\frac{V_4}{R_2}$$

$$\Rightarrow j\omega C_2 V = -\frac{V_4}{R_2} \Rightarrow V = -\frac{V_4}{j\omega R_2 C_2}$$

a) Replace V in $\textcircled{1}$ with V in $\textcircled{2}$,

$$V_1 = -V_4 \left(\frac{j\omega R_1 C_1 + j\omega R_1 C_2 + 1 - \omega^2 R_1 R_2 C_1 C_2}{j\omega R_2 C_2} \right)$$

$$\frac{V_4}{V_1} = -\frac{j\omega R_2 C_2}{j\omega R_1 C_1 + j\omega R_1 C_2 + 1 - \omega^2 R_1 R_2 C_1 C_2}$$

$$= -\frac{1}{R_1 \left(\frac{C_1 + C_2}{R_2 C_2} \right) + j \left(R_1 C_1 \omega - \frac{1}{\omega R_2 C_2} \right)}$$

$$c) \left| \frac{V_4}{V_1} \right| = \frac{1}{\sqrt{\left\{ R_1 \left(\frac{C_1 + C_2}{R_2 C_2} \right)^2 \right\}^2 + \left(R_1 C_1 \omega - \frac{1}{\omega R_2 C_2} \right)^2}}$$

$\left| \frac{V_4}{V_1} \right|$ goes to 0 when $\begin{cases} \omega \rightarrow 0 \\ \omega \rightarrow \infty \end{cases}$

∴ Band pass filter

To find bandwidth with half power frequencies,

$$\omega R_1 C_1 - \frac{1}{\omega R_2 C_2} = \pm R_1 \frac{C_1 + C_2}{R_2 C_2}$$


$$\Rightarrow \omega^2 \pm \frac{C_1 + C_2}{R_2 C_1 C_2} \omega - \frac{1}{R_1 R_2 C_1 C_2} = 0$$

$$\text{Let } A = \frac{C_1 + C_2}{R_2 C_1 C_2}, \quad B = -\frac{1}{R_1 R_2 C_1 C_2}$$

$$\omega_1, \omega_2 = \frac{1}{2} \left(\pm A + \sqrt{A^2 - 4B} \right) \quad (\omega_1, \omega_2 > 0 \quad \sqrt{A^2 - 4B} > A)$$

$$\therefore \omega_2 - \omega_1 = A = \frac{C_1 + C_2}{R_2 C_1 C_2} \quad (\text{rad/msec})$$

1. [20 points] 다음 RLC 회로에 대한 물음에 답하여라.

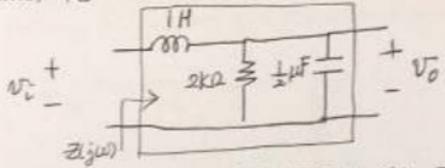

(a) [10 points] 등가 임피던스가 실수가 되도록 하는 공진 주파수 ω 를 구하여라. Find the resonance frequency (ω) to make the equivalent impedance be real.

$$\begin{aligned} Z(j\omega) &= j\omega L + \left(2 \parallel \frac{1}{j\omega C}\right) \Rightarrow L=1, C=\frac{1}{2} \\ &= j\omega + \frac{2}{1+j\omega} = j\omega + \frac{2(1-j\omega)}{1+\omega^2} = j\omega + \frac{2}{1+\omega^2} - \frac{2j\omega}{1+\omega^2} \\ &= \left(\omega - \frac{2\omega}{1+\omega^2}\right)j + \frac{2}{1+\omega^2} \end{aligned}$$


$$\omega = \frac{2\omega}{1+\omega^2} \rightarrow \omega^3 = \omega \rightarrow \omega = \underbrace{1}_{\text{rad/ms}}$$

(b) [10 points] 이 회로의 주파수 응답 $H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$ 을 구하고 크기 $|H(j\omega)|$ 를 극사적으로 도시 하여라. Find the frequency response of the circuit, $H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$ and sketch the magnitude plot $|H(j\omega)|$. Hint: Find the values at ($\omega = 0, \infty$, resonance frequency)


$$\begin{aligned} H(j\omega) &= \frac{2 \parallel \frac{1}{j\omega C}}{j\omega L + (2 \parallel \frac{1}{j\omega C})} = \frac{\frac{2}{1+j\omega}}{j\omega + \frac{2}{1+j\omega}} = \frac{2}{2+j\omega(1+j\omega)} \\ &= \frac{2}{2-\omega^2+j\omega} \end{aligned}$$

$$\therefore |H(j\omega)| = \frac{2}{\sqrt{(2-\omega^2)^2 + \omega^2}}$$
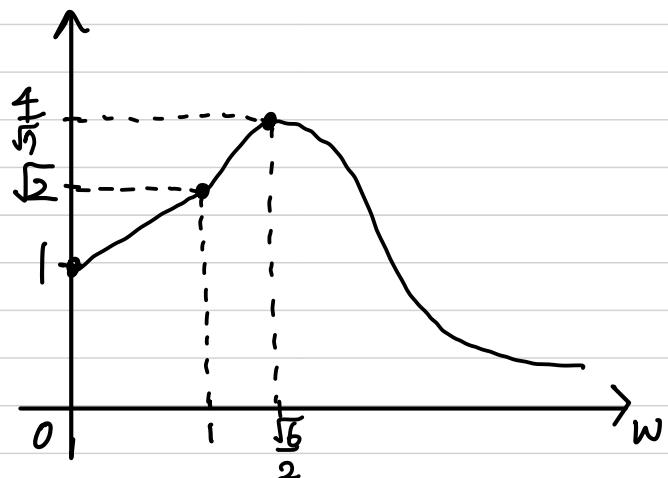
$$\therefore \begin{cases} \omega \rightarrow 0 & : 1 \\ \omega \rightarrow \infty & : 0 \\ \omega \rightarrow 1 & : \sqrt{2} \\ \omega \rightarrow \frac{\sqrt{6}}{2} & : \frac{4}{\sqrt{5}} \end{cases}$$




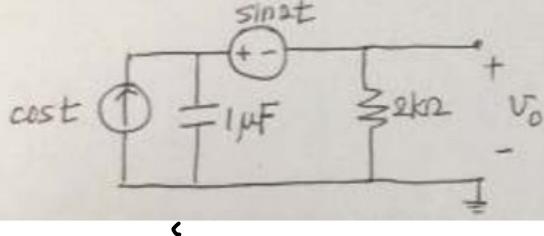2. [10 points] 다음 회로에서 sinusoidal steady state에서의 출력 전압을 구하여라.



Use superposition.
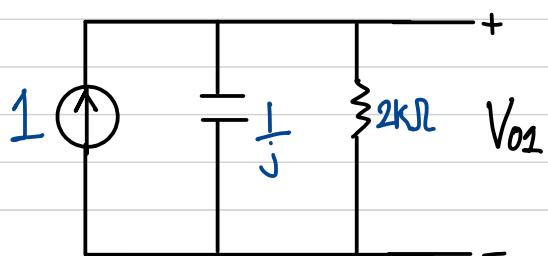
$$\textcircled{1} \cos t = \operatorname{Re}(e^{jt})$$




$$V_{o1} = \left(\frac{1}{j} // 2 \right) \cdot 1 = \frac{2}{1+j2}$$

$$\therefore V_{o1}(t) = \frac{2}{\sqrt{5}} \cos(t - \theta_1), \tan \theta_1 = 2$$

$$\textcircled{2} \sin 2t$$
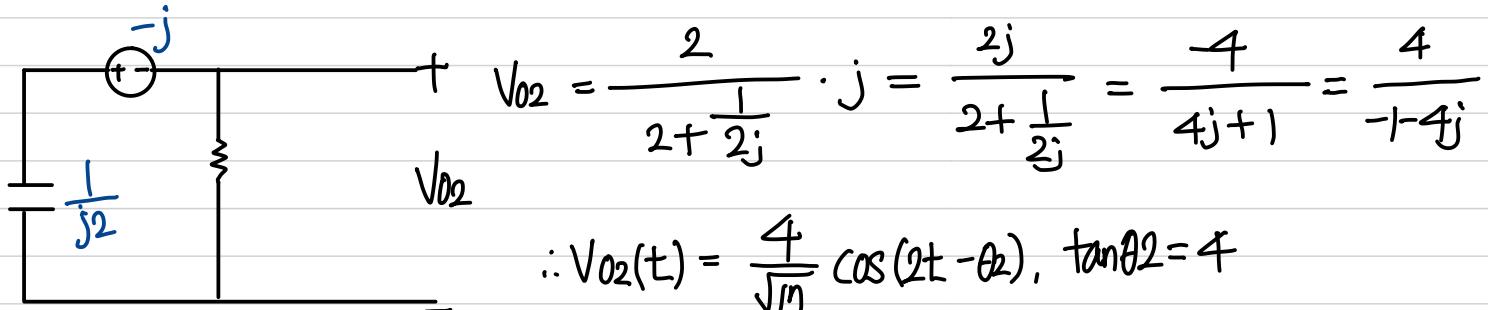
$$\sin 2t = \cos(2t - \frac{\pi}{2}) = \operatorname{Re}(e^{j(2t - \frac{\pi}{2})}) \Rightarrow -j$$



$$V_{o2} = \frac{2}{2 + \frac{1}{2j}} \cdot j = \frac{2j}{2 + \frac{1}{2j}} = \frac{-4}{4j+1} = \frac{4}{-1-4j}$$

$$\therefore V_{o2}(t) = \frac{4}{\sqrt{17}} \cos(2t - \theta_2), \tan \theta_2 = 4$$

$$\therefore V_o(t) = V_{o1}(t) + V_{o2}(t) = \frac{2}{\sqrt{5}} \cos(t - \theta_1) + \frac{4}{\sqrt{17}} \cos(2t - \theta_2), \tan(\theta_1) = 2, \tan(\theta_2) = 4$$