

Homework # 1

Due date: Sept. 27 (Tuesday)

[Textbook]

Prob. 1.2

Exercise 2.3 (d), 2.8 (c)

Problem 2.9, 2.11 (b)

Exercise 3.10, 3.16, 3.25


Problem 3.3, 3.6

[Previous exams] 2019. 1st exam


2. [20 points] 아래 회로에 답하여라. (show the equations you use)

(a) [10 points] 아래 회로에서 노드 분석법을 이용하여 v 를 구하여라. Find v with the node analysis.

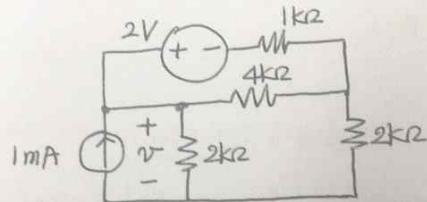(b) [10 points] 아래 회로에서 메쉬(루프) 분석법을 이용하여 v 를 구하여라. Find v with the mesh(loop) analysis.




3. [15 points] 다음 회로에 대한 Thevenin 등가회로를 구하여라. Find the Thevenin equivalent circuit of the following circuit.

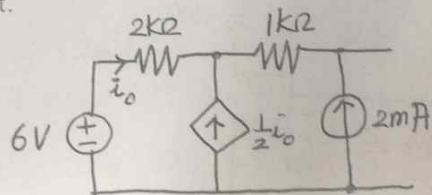


Problem 1.2

PROBLEM 1.2 Sketch the $v-i$ characteristic of a battery rated at 10 V with an internal resistance of 10 Ohms.

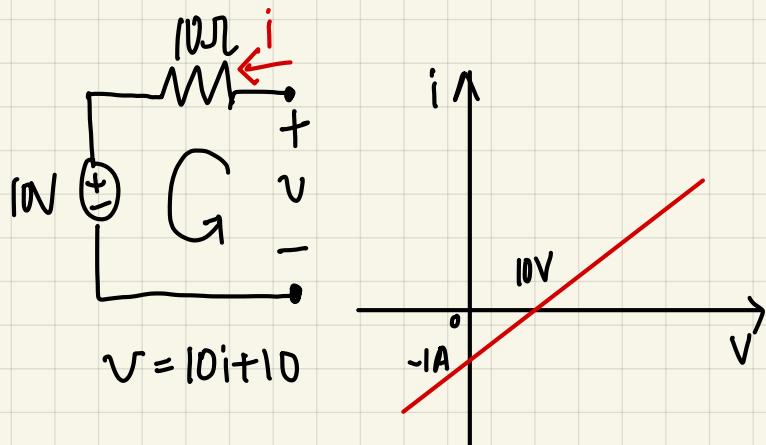

Exercise 2.3 (d)

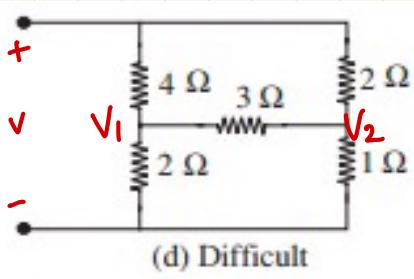


Node analysis.


$$V_1: \frac{V_1 - V}{4} + \frac{V_1 - V_2}{3} + \frac{V_1}{2} = 0 \rightarrow 13V_1 - 3V - 4V_2 = 0$$

$$V_2: \frac{V_2 - V}{2} + \frac{V_2 - V_1}{3} + \frac{V_2}{1} = 0 \rightarrow -2V_1 - 3V + 11V_2 = 0$$

$V_1 = V_2 = \frac{1}{3}V \rightarrow$ No current flows through 3Ω .

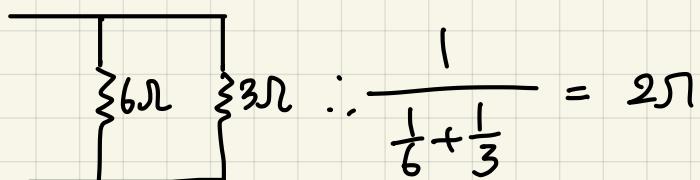


Exercise 2.8 (c)

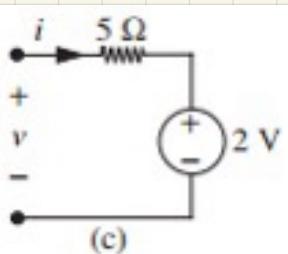


$$V = 5i + 2$$

$$i = \frac{1}{5}V - \frac{2}{5}$$

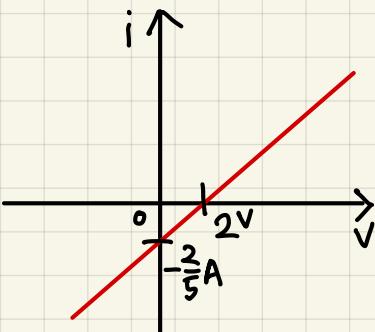

Problem 2.9

Sol② Node analysis

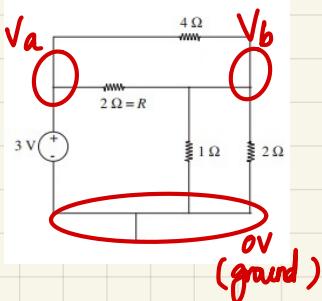

$$V_a = 3V$$

$$\frac{V_b - 3}{2} + \frac{V_b - 3}{4} + \frac{V_b}{2} + \frac{V_b}{1} = 0 \rightarrow V_b = 1V$$

Voltage at Resistor R : $V_a - V_b = 2V$

$$P = \frac{V^2}{R} = \frac{4}{2} = 2W$$

Problem 2.11(b)



Let I current in this circuit, then

$$I = \frac{V_s}{R_s + R_L}$$

Let P_L power dissipated in R_L , then

$$P_L = I^2 \cdot R_L$$

$$= \frac{V_s^2}{(R_s + R_L)^2} \cdot R_L$$

$$\frac{\partial P_L}{\partial R_L} = V_s^2 \left\{ \frac{1}{(R_s + R_L)^2} + \frac{-2R_L}{(R_s + R_L)^3} \right\}$$

$$= V_s^2 \cdot \frac{R_s - R_L}{(R_s + R_L)^3}$$


$$\text{Let } \frac{\partial P_L}{\partial R_L} = 0, \quad R_3 = R_L$$

$$\text{If } R_3 < R_L, \quad \frac{\partial P_L}{\partial R_L} < 0$$

$$\text{If, } R_3 > R_L, \quad \frac{\partial P_L}{\partial R_L} > 0$$

$\therefore P_L$ is maximized when $R_3 = R_L$ \square

Ex 3.10

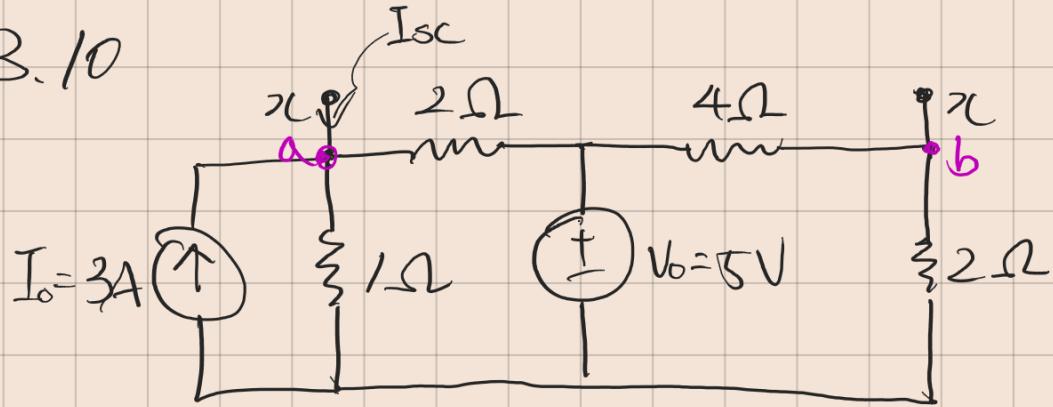

Set $I_o = 0$, $V_o = 0$, then

$$R_{TH} = 1//2 + 4//2$$

$$= \frac{1 \cdot 2}{1+2} + \frac{4 \cdot 2}{4+2} = 2 \Omega$$

Use node analysis, then

$$\text{For } a, 3 = \frac{V_a - 0}{1} + \frac{V_a - 5}{2}$$

$$\therefore V_a = \frac{11}{3} V$$


$$\text{For } b, \frac{5 - V_b}{4} = \frac{V_b - 0}{2}$$

$$\therefore V_b = \frac{5}{3} V$$

$$V_{oc} = V_a - V_b = \frac{11}{3} - \frac{5}{3} = 2 V$$

$$I_{sc} = \frac{V_{oc}}{R_{TH}} = 1 A$$

\therefore Norton equivalent

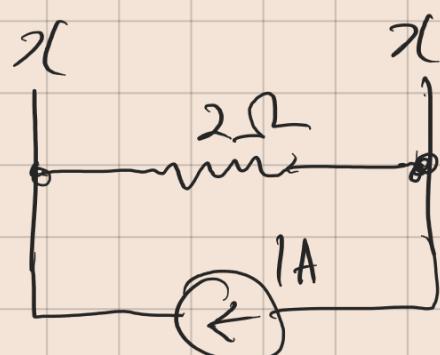

Ex 3.16

1) Set V_1, V_2 as 0

Let V' voltage across R_2


No current through R_2



$$\therefore V' = 0 \text{ V}$$

2) Set V_1, I as 0



Let V'' voltage across R_2

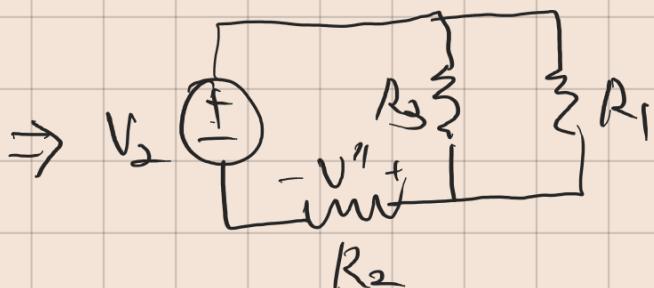

$$V'' = \frac{R_2}{R_1 // R_3 + R_2} V_2$$

3) Set V_2, I as 0

Let V''' voltage across R_2

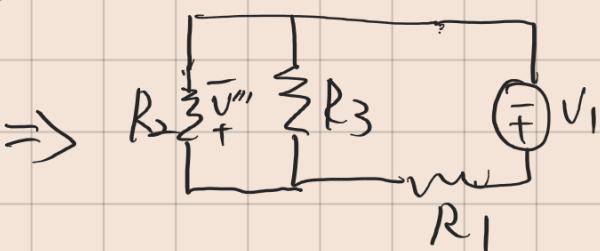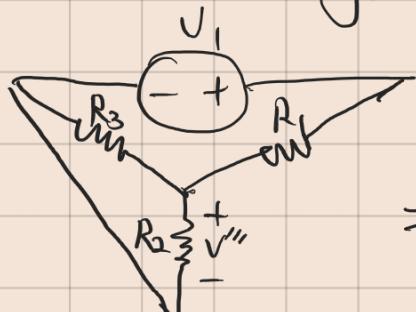

$$V''' = \frac{R_2 // R_3}{R_1 + R_2 // R_3} \cdot V_1$$

$$\therefore V = V' + V'' + V'''$$

$$= \frac{R_2}{R_1 // R_3 + R_2} V_2 + \frac{R_2 // R_3}{R_1 + R_2 // R_3} V_1$$

EXERCISE 3.25 Find the node potential E in Figure 3.128.


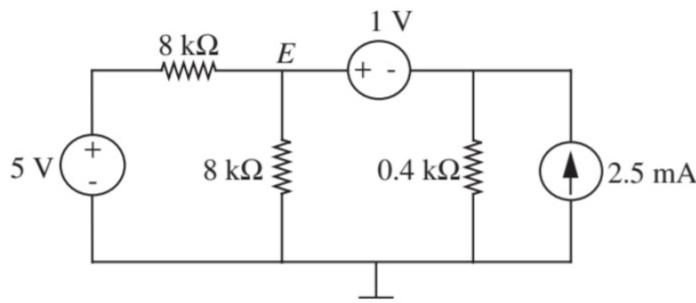


Figure 3.128

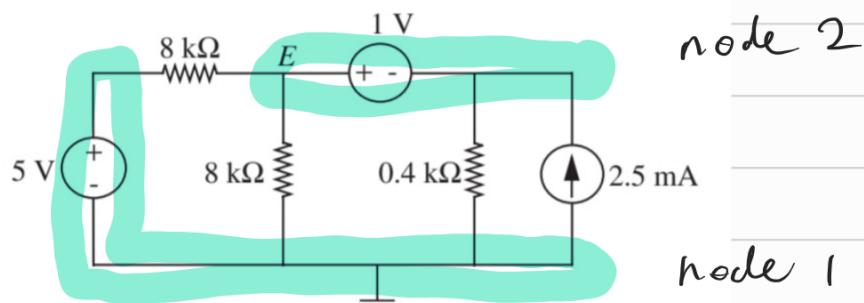Label the nodes node 1 & node 2 as follows:



By the node analysis, we get the following equation:

$$\frac{E-5}{8} + \frac{E}{8} + \frac{E-1}{0.4} = 2.5$$

$$E - 5 + E + 20(E-1) = 20$$

$$22E = 45$$

$$\therefore E = \frac{45}{22} \text{ (V)}$$

PROBLEM 3.3 Find V_0 in Figure 3.132. Solve by (1) node method, (2) superposition. All resistances are in ohms.


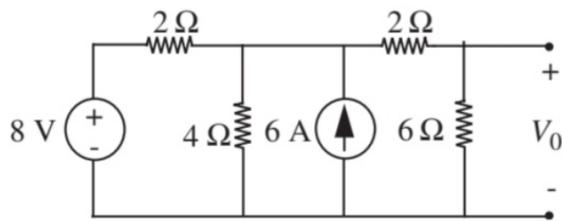


Figure 3.132

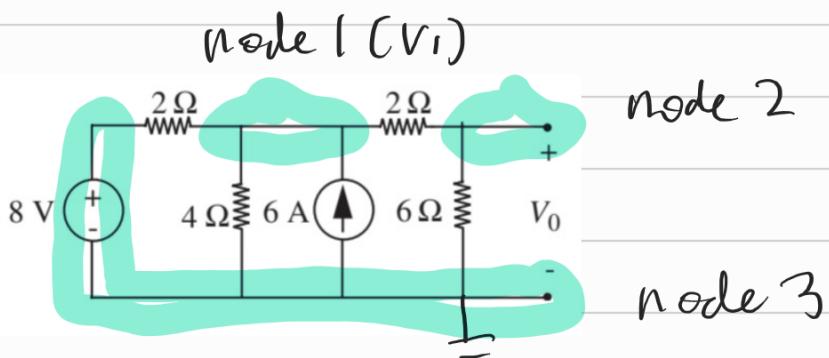(1) node method

First, choose one of nodes in the circuit as a reference node.

And then label the nodes node 1, node 2, and node 3 as follows:



By the node analysis, we get the following two equations:

from node 1,

$$\frac{V_1 - 8}{2} + \frac{V_1}{4} + \frac{V_1 - V_0}{2} = 6 \quad \dots \textcircled{1}$$

from node 2,

$$\frac{V_1 - V_0}{2} = \frac{V_0}{6} \quad \dots \textcircled{2}$$

From eqn. ②, we get:

$$3V_1 - 3V_o = V_o$$

$$\therefore V_1 = \frac{4}{3} V_o \dots \textcircled{3}$$

Substituting V_1 in ① with ③, we get:

$$\frac{2V_o}{3} - 4 + \frac{V_o}{3} + \frac{V_o}{6} = 6$$

$$4V_o - 24 + 2V_o + V_o = 36$$

$$7V_o = 60$$


$$\therefore V_o = \frac{60}{7} \text{ (V)}$$

(2) Superposition


Since the given circuit is a linear circuit, we can compute the contribution of each voltage / current in V_o by the superposition principle.

① contribution of the 8V voltage source (V_{o1})

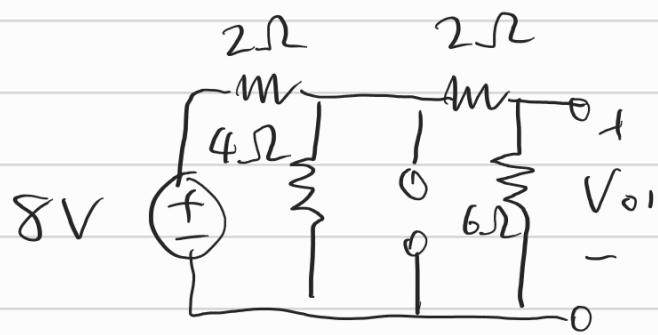To ignore the effect of the current source, substitute it with an open circuit



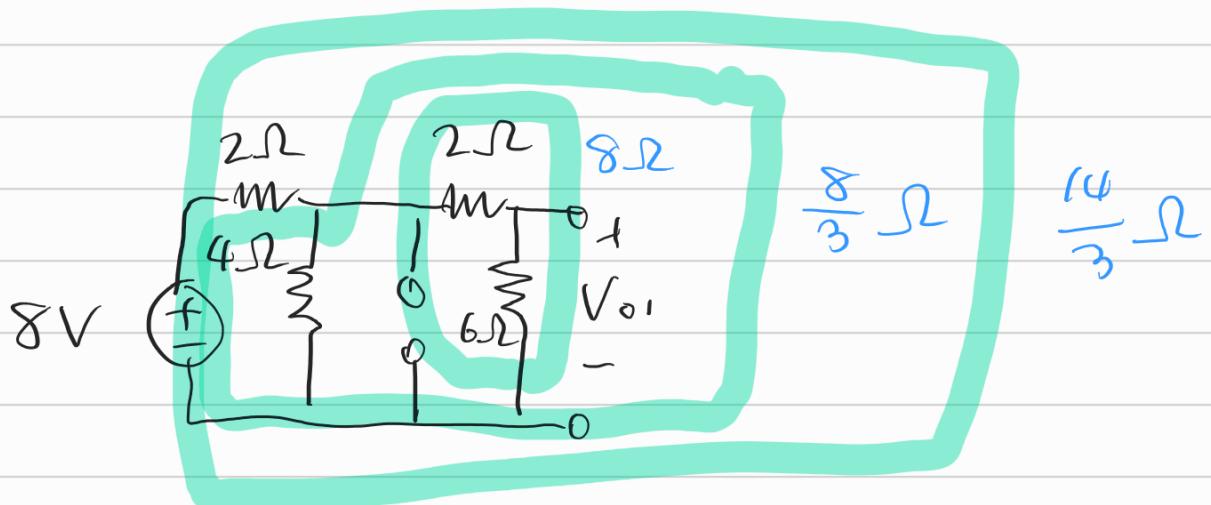
Now, we can find equivalent resistances for some groups of resistors as follows:




$$V_{o1} = 8 \times \frac{\frac{8}{3}}{\frac{14}{3}} \times \frac{6}{8} = \frac{24}{7} (V)$$

② contribution of the 6A current source (V_{o2})

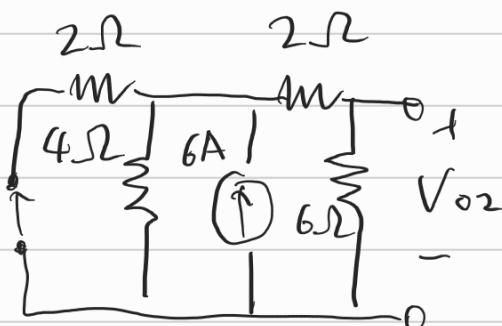In a similar way to ①, we substitute the voltage source with a short circuit



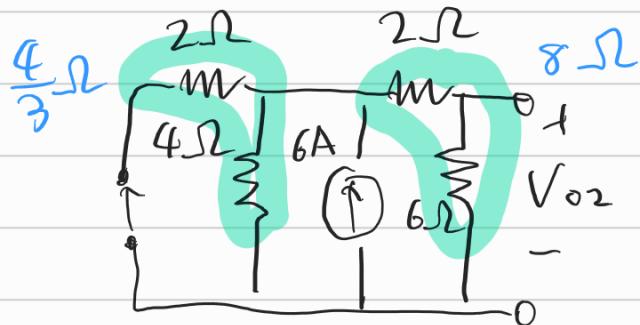Now, we can find equivalent resistance for groups of resistors as follows:



Then, we get :

$$V_{o2} = 6 \times \frac{\frac{4}{3}}{\frac{4}{3} + 8} \times 6$$

$$= 36 \times \frac{1}{7} = \frac{36}{7} (V)$$

Finally, by the superposition principle, we get:

$$V_o = V_{o1} + V_{o2} = \frac{24}{7} + \frac{36}{7} = \frac{60}{7} (V)$$

PROBLEM 3.6 Find v_i for $I = 3 \text{ A}$, $V = 2 \text{ V}$ in Figure 3.135. Strategy: To avoid numerical errors, derive expressions in literal form first, then check dimensions.


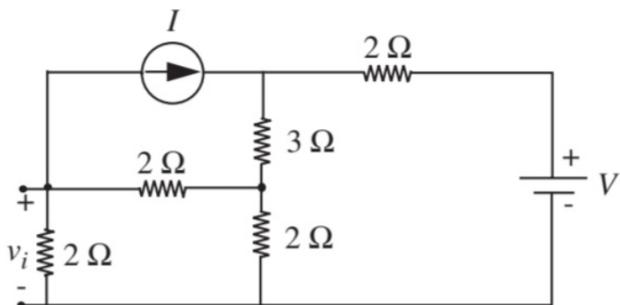


Figure 3.135

We can use the mesh analysis method

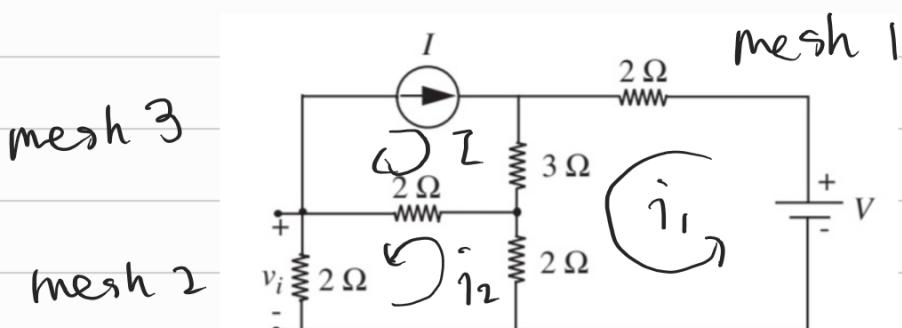Label the meshes mesh 1, 2, and 3 as follows:



By the mesh analysis, we get the following 2 equations:

From mesh 1,

$$2i_1 + 3(i_1 + I) + 2(i_1 - i_2) = V$$

$$\Rightarrow 7i_1 - 2i_2 = V - 3I \quad \dots \textcircled{1}$$

From mesh 2,

$$2(i_2 - i_1) + 2(i_2 + I) + 2i_2 = 0$$

$$\Rightarrow 3i_2 - i_1 = -I \quad \dots \textcircled{2}$$

From ① and ②, we get

$$7(3i_2 + L) - 2i_2 = 19i_2 + 7L = V - 3L$$

$$\therefore i_2 = \frac{V - 10L}{19}$$

Since $V_i = 2i_2$, we finally get:

$$V_i = 2i_2 = \frac{2V - 20L}{19} = \frac{2 \cdot 2 - 20 \cdot 3}{19}$$

$$= -\frac{56}{19} (V)$$

prev exam

2. (a) node analysis

Solution

Let C be a reference node

then, $V_C = 0$, $V_a = V$

① KCL at b.

$$\frac{(V - V_b)}{1} + \frac{V - V_b}{4} + \frac{0 - V_b}{2} = 0$$

$$\Rightarrow 5V - 7V_b = 8$$


② KCL at c

$$-1 + \frac{V}{2} + \frac{V_b}{2} = 0$$

$$\Rightarrow V + V_b = 2 \Rightarrow 7V + 7V_b = 14$$

from ① and ②

$$\therefore V = \frac{14}{6} V$$

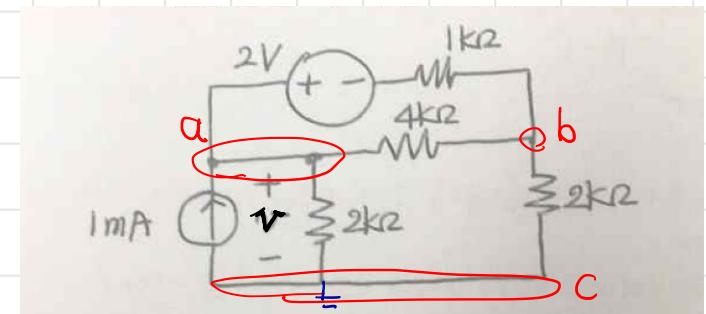

2. (b) mesh (loop) analysis

Solution

① KVL at mesh 1

$$2 + \bar{i}_1 + 4(\bar{i}_1 - \bar{i}_2) = 0$$

$$\Rightarrow 5\bar{i}_1 - 4\bar{i}_2 = -2$$

② KVL at mesh 2


$$2(\bar{i}_2 - 1) + 4(\bar{i}_2 - \bar{i}_1) + 2\bar{i}_2 = 0$$

$$\Rightarrow -4\bar{i}_1 + 8\bar{i}_2 = 2$$

from ① and ② $\bar{i}_2 = \frac{1}{12}$

$$V = 2(-\bar{i}_2)$$

$$\therefore V = \frac{14}{6} V$$

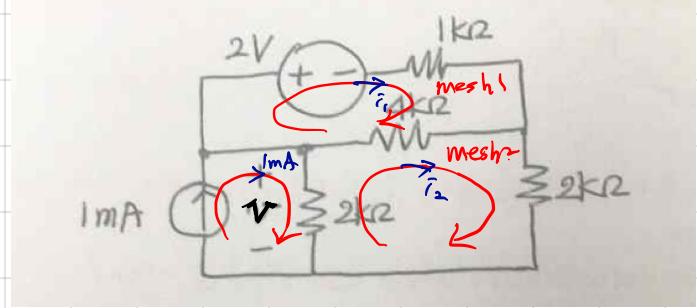

prev exam

3. Thevenin equivalent circuit

Solution 1

① KVL at loop 1

$$-b + 2\tau_o + \frac{3}{2}\tau_o + V = 0$$

$$\Rightarrow V = -\frac{1}{2}\tau_o + b$$

② KCL at a

$$I + \frac{3}{2}\tau_o + 2 = 0$$


$$\Rightarrow \tau_o = -\frac{2}{3}(I+2)$$

from ① and ②

$$V = \left(-\frac{1}{2}\right) \cdot \left(-\frac{2}{3}\right)(I+2) + b.$$

$$\Rightarrow V = \frac{1}{3}I + \frac{32}{3}$$

$$V = R_{TH}I + V_{TH}$$

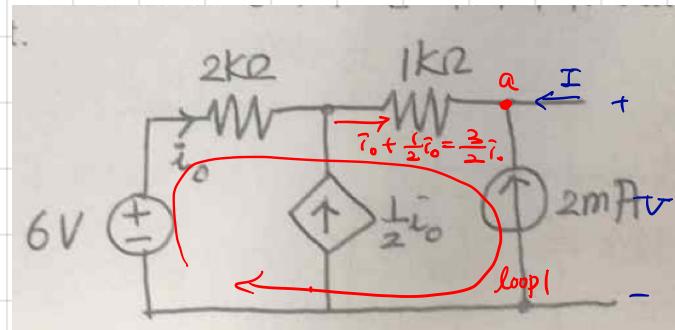

$$\therefore V_{TH} = \frac{32}{3} \text{ V}, R_{TH} = \frac{1}{3} \text{ kΩ}$$

Solution 2

To get V_{TH}

Let C be a reference node.

$$\text{then } V_c = 0, V_d = 6, V_a = -V_{oc}$$

① KCL at a.

$$\frac{V_b - V_{oc}}{1} + 2 = 0$$

$$\Rightarrow -V_{oc} = V_b + 2$$

② KCL at C

$$\tau_o + \frac{1}{2}\tau_o + 2 = 0$$

$$\Rightarrow \tau_o = -\frac{4}{3}$$


③ KCL at d.

$$\tau_o + \frac{V_b - b}{2} = 0$$

$$\Rightarrow V_b = -2\tau_o + b = (-2)(-\frac{4}{3}) + b = \frac{26}{3}$$

from ① and ③
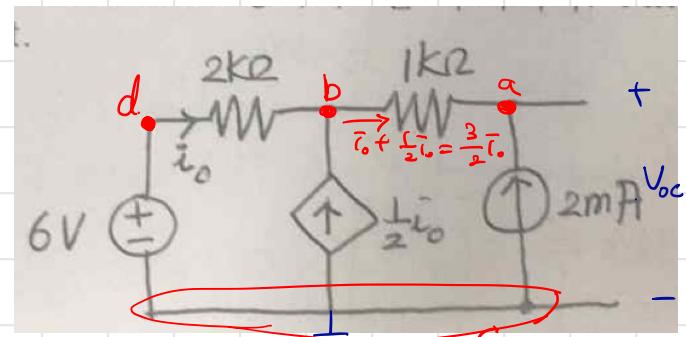
$$\therefore V_{oc} = \frac{32}{3} \text{ V} = V_{TH}$$



To get R_{th}

① KVL at loop 1

$$-6 + 2\bar{I}_o + \frac{3}{2}\bar{I}_o = 0$$

$$\Rightarrow \frac{7}{2}\bar{I}_o = 6 \Rightarrow \bar{I}_o = \frac{12}{7}$$

② KCL at a

$$\frac{3}{2}\bar{I}_o + 2 - I_{sc} = 0$$

from ① and ②

$$I_{sc} = \frac{3}{2} \cdot \frac{12}{7} + 2 = \frac{32}{7}$$

$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{\frac{32}{3}}{\frac{32}{7}}$$

$$\therefore R_{th} = \frac{7}{3} k\Omega$$

