

Homework # 2

Due date: Oct. 11 (Tuesday)

[Textbook]

Exercise 4.4

Problem 4.4, 4.13

Exercise 5.8

Problem 5.10


Exercise 6.3 (a) (b)

[Previous exams] 2019. 1<sup>st</sup> exam

4. [15 points] 다음 다이오드에 대한 물음에 답하여라. Answer the following questions for the diode circuit below.

(a) [10 points] 이상적인 다이오드의 경우 출력 파형을 도시하여라. Draw the output waveform assuming that all diodes are ideal. (힌트 Hint: First assume that both diodes are turned-off to get the output waveform and find the range of input voltage that satisfies the assumption)

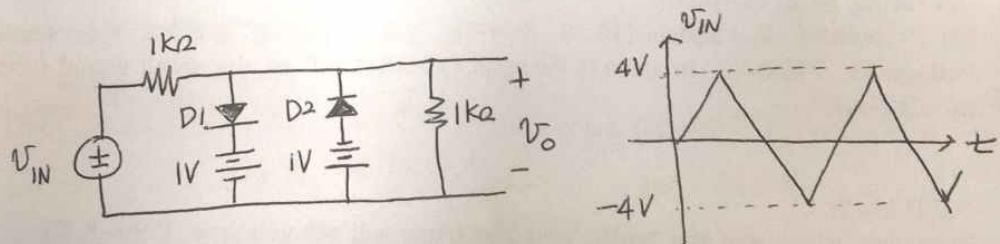(b) [5 points] 다이오드의 turn-on 전압이 0.6V 인 경우의 출력 파형을 도시하여라. Draw the output waveform when the turn-on voltage of each diode is 0.6V.



### Exercise 4.4

#### EXERCISE 4.4

- a) Plot the  $i_A$  vs.  $v_A$  characteristics for the nonlinear network shown in Figure 4.49.  
Assume the diode is ideal.


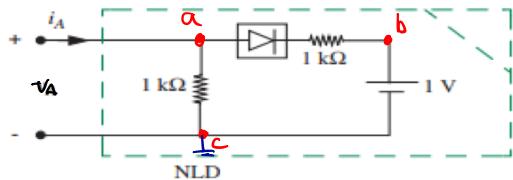


FIGURE 4.49

Solution


Let  $c$  be a reference node, then,  $V_c = 0$ ,  $V_b = 1$

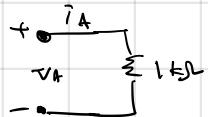① If  $V_a < V_b = 1$ , the diode is off. (open circuit)




$$V_A = 1 \cdot I_A \Rightarrow \bar{I}_A = V_A$$

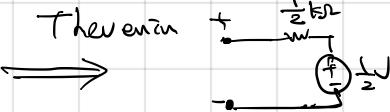② If  $V_a \geq V_b = 1$ , the diode is on. (short circuit)



$$V_A = \frac{1}{2} \bar{I}_A + \frac{1}{2}$$

$$\Rightarrow \bar{I}_A = 2V_A - 1$$

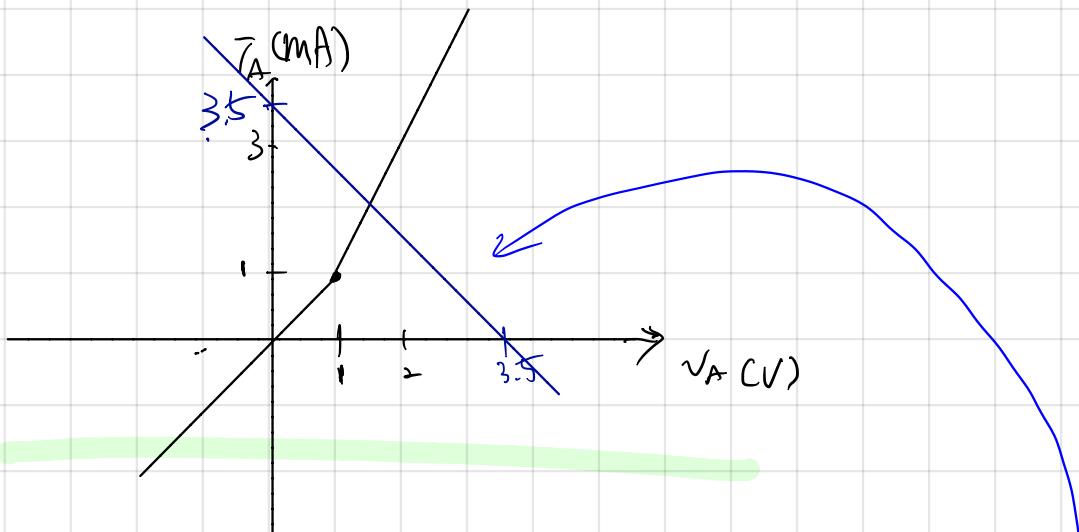

- b) The nonlinear network from part (a) is connected as shown in Figure 4.50. Draw the load line on your  $v$ - $i$  characteristics from part (a), and find  $i_T$ .

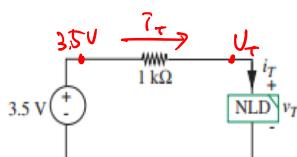


FIGURE 4.50

Solution

$$\bar{I}_T = \frac{3.5 - V_T}{1} = -V_T + 3.5$$

$$\bar{I}_T = -V_T + 3.5 = 2V_T - 1$$

$$\Rightarrow V_T = 1.5$$

$$\therefore \bar{I}_T = 2 \text{ mA.}$$

### Problem 4.4

- a) Assuming the diode can be modeled as an ideal diode, and  $R_1 = R_2$ , plot the waveform  $v_o(t)$  for the circuit in Figure 4.18, assuming a triangle wave input. Write an expression for  $v_o(t)$  in terms of  $v_i$ ,  $R_1$  and  $R_2$ .
- b) If the triangle wave has a peak amplitude of only 2 volts, and  $R_1 = R_2$ , a more accurate diode model must be used. Plot and write an expression for  $v_o$  assuming that the diode is modeled using an ideal diode in series with a 0.6 volt source. Draw the transfer curve  $v_o$  versus  $v_i$ .


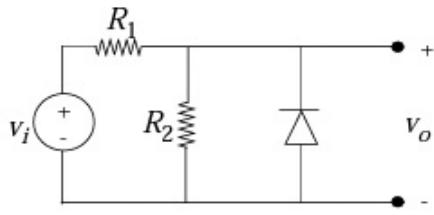
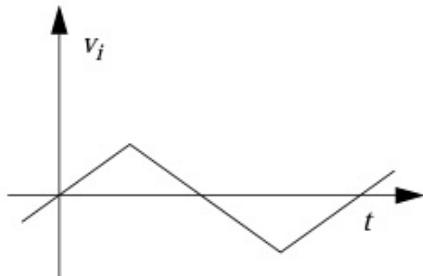



Figure 4.18:

(a) ① Diode off :  $i_D = 0, V_D > 0$


$$V_o = V_D, \boxed{V_o > 0}$$

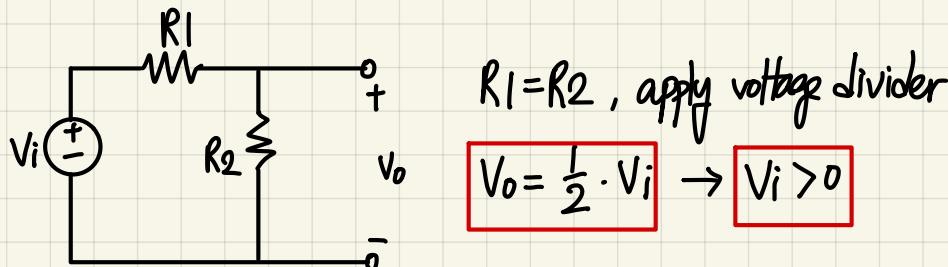


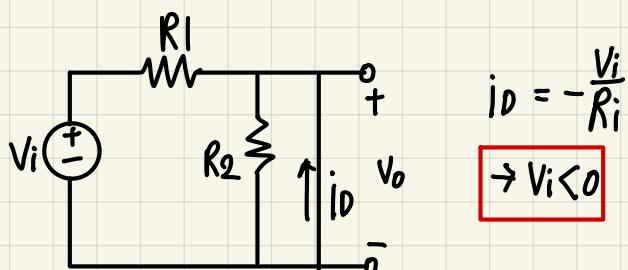② Diode on :  $i_D > 0, V_D = 0 \rightarrow \boxed{V_o = 0}$



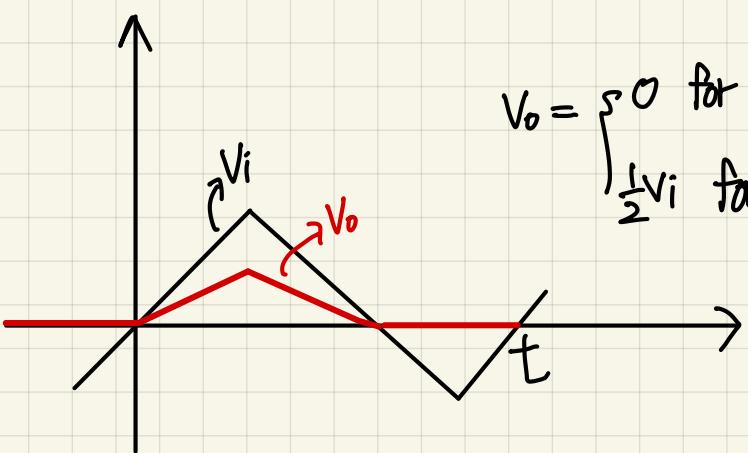
$$V_o = \begin{cases} 0 & \text{for } V_i < 0 \\ \frac{1}{2}V_i & \text{for } V_i \geq 0 \end{cases}$$



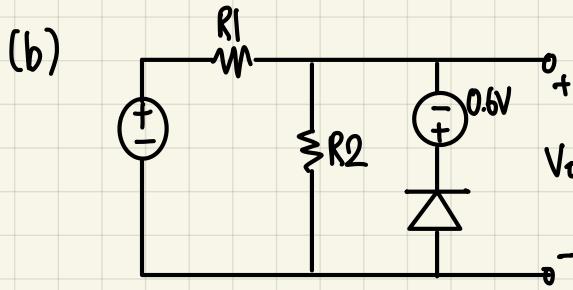


① Diode off :  $i_D = 0, V_D > 0$

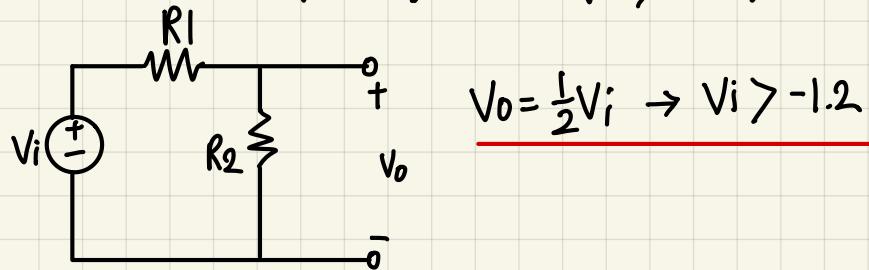
$$V_0 = V_D - 0.6 \rightarrow V_0 > -0.6V$$



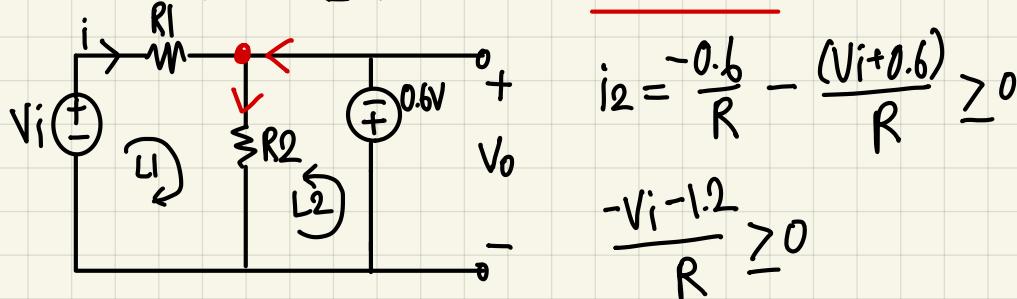② Diode on :  $i_D \geq 0, V_D = 0 \rightarrow V_0 = -0.6V$



$$\underline{V_i \leq -1.2}$$

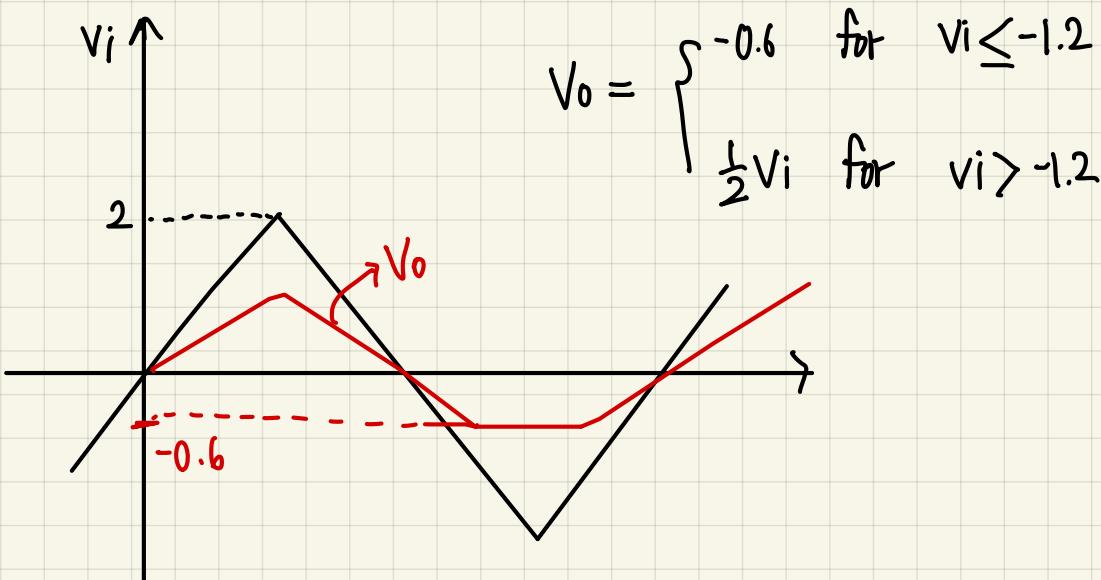

**Problem 4.13** The circuit shown in Figure 4.31 contains a nonlinear element with the following properties:


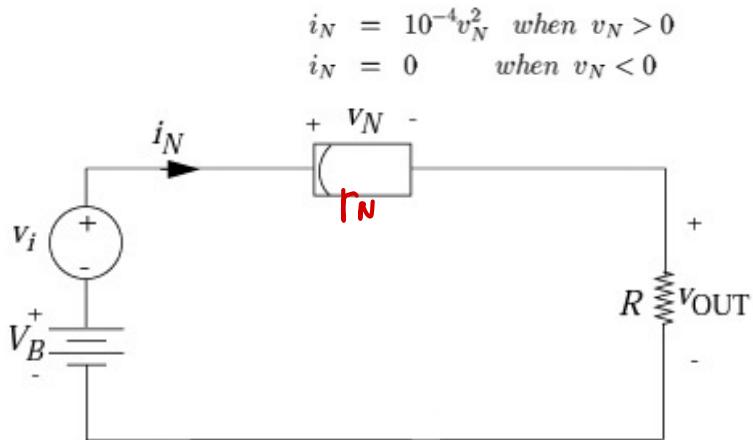


Figure 4.31:


$$\text{assume } V_i = 10^{-3} \sin(\omega t), \quad V_N = 10V, \quad i_N = 10^{-4} V_N^2$$

$$\frac{di_N}{dv_N} = 2 \times 10^{-4} V_N$$
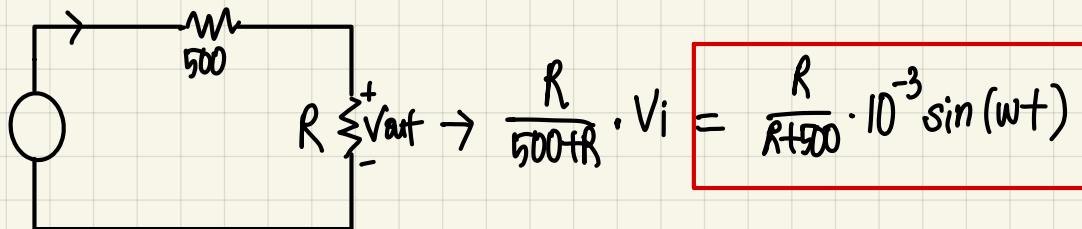
$$\text{at } V_N = 10, \quad \frac{di_N}{dv_N} = \frac{1}{500} = \frac{1}{R_N} \rightarrow R_N = 500$$



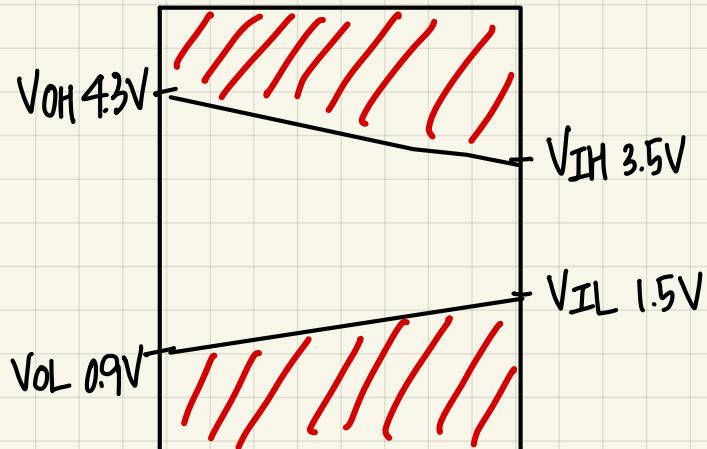**Exercise 5.8** A logic gate obeys a static discipline with the following voltage levels:  $V_{IH} = 3.5V$ ,  $V_{OH} = 4.3V$ ,  $V_{IL} = 1.5V$  and  $V_{OL} = 0.9V$ . (a) What range of voltages will be treated as invalid under this discipline? (b) What are its noise margins?



(a) Output voltages ,

$$0.9V < V < 4.3V$$

will be treated as invalid.


Input voltages

$$1.5V < V < 3.5V$$

$$(b) NM_0 = V_{IL} - V_{OL} = 0.6V$$

$$NM_1 = V_{OH} - V_{IH} = 0.8V$$

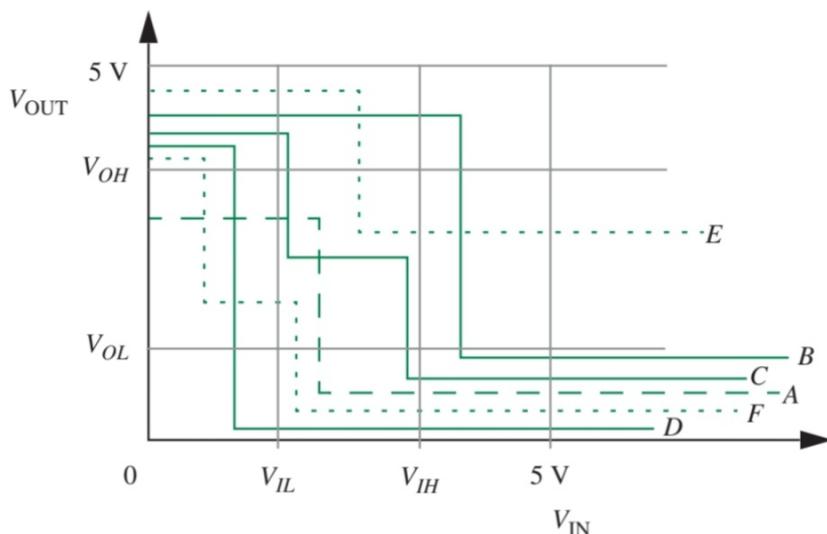**PROBLEM 5.10** Figure 5.42 illustrates input-output voltage transfer functions for several one-input one-output devices. For the voltage thresholds  $V_{OL}$ ,  $V_{IL}$ ,  $V_{OH}$ , and  $V_{IH}$  as shown, which of the devices can serve as valid inverters?



An inverter is a device that outputs a voltage representing the opposite logic-level to its input (i.e.  $0 \rightarrow 1$  and  $1 \rightarrow 0$ ).

input  $\rightarrow$  output


input	output
0	1
1	0

To serve as a valid inverter, a device must output a valid voltage for logical 1 if the input voltage is logical 0 and logical 0 if the input voltage is logical 1.

That is, a circuit must satisfy the following conditions:

$$0V \leq V_{IN} \leq V_{IL} \Rightarrow V_{OH} \leq V_{OUT} \leq 5V$$
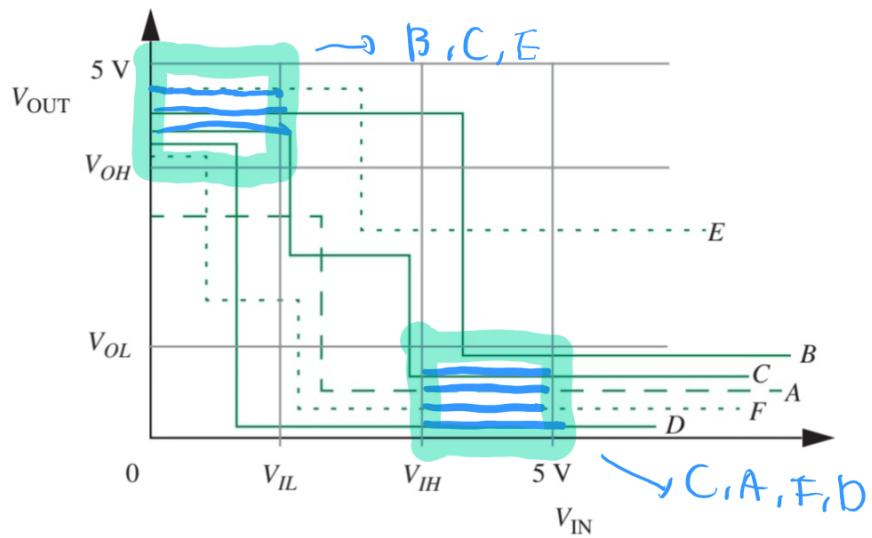
$$V_{IH} \leq V_{IN} \leq 5V \Rightarrow 0V \leq V_{OUT} \leq V_{OL}$$




Among the given devices, only C can serve as a valid inverter.

**EXERCISE 6.3** Figure 6.60 shows an inverter circuit using a MOSFET and a resistor. The MOSFET has a threshold voltage  $V_T = 2 \text{ V}$ . Assume that  $V_S = 5 \text{ V}$  and  $R_L = 10 \text{k}\Omega$ . For this exercise, model the MOSFET using its switch model. In other words, assume that the on-state resistance of the MOSFET is 0.

- a) Draw the input versus output voltage transfer curve for the inverter.

Case 1.  $V_{IN} < V_T$

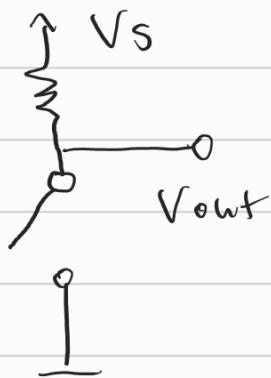

Case 2.  $V_{IN} > V_T$


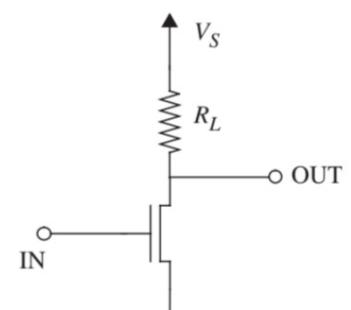
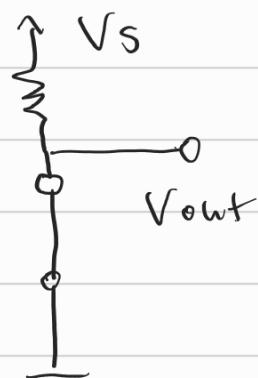


FIGURE 6.60

$$V_{out} = V_S$$

$$V_{out} = 0$$

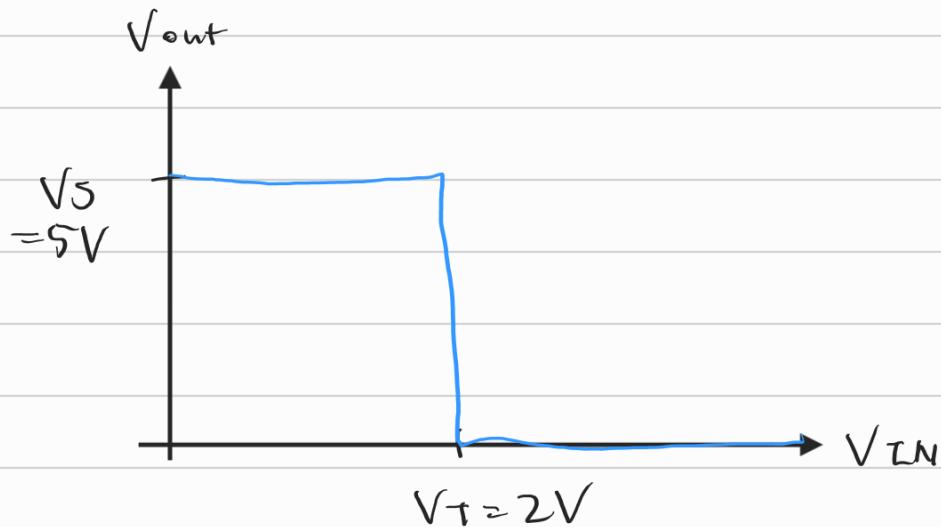


- b) Does the inverter satisfy the static discipline for the voltage thresholds  $V_{OL} = 1$  V,  $V_{IL} = 1.5$  V,  $V_{OH} = 4$  V and  $V_{IH} = 3$  V? Explain. (Hint: To satisfy the static discipline, the inverter must interpret correctly input values that are valid logic signals. Furthermore, given valid logic inputs, the inverter must also output valid logic signals. Valid logic 0 input signals are represented by voltages less than  $V_{IL}$ , valid logic 1 input signals are represented by voltages greater than  $V_{IH}$ , valid logic 0 output signals are represented by voltages less than  $V_{OL}$ , and valid logic 1 output signals are represented by voltages greater than  $V_{OH}$ .)

The answer is "yes".

$$\text{When } 0V \leq V_{IN} \leq V_{IL} = 1.5V, \quad V_{OUT} = 5V > V_{OH} = 4V.$$

$$\text{When } V_{IN} \geq V_{IH} = 3V, \quad V_{OUT} = 0V < V_{OL} = 1V$$

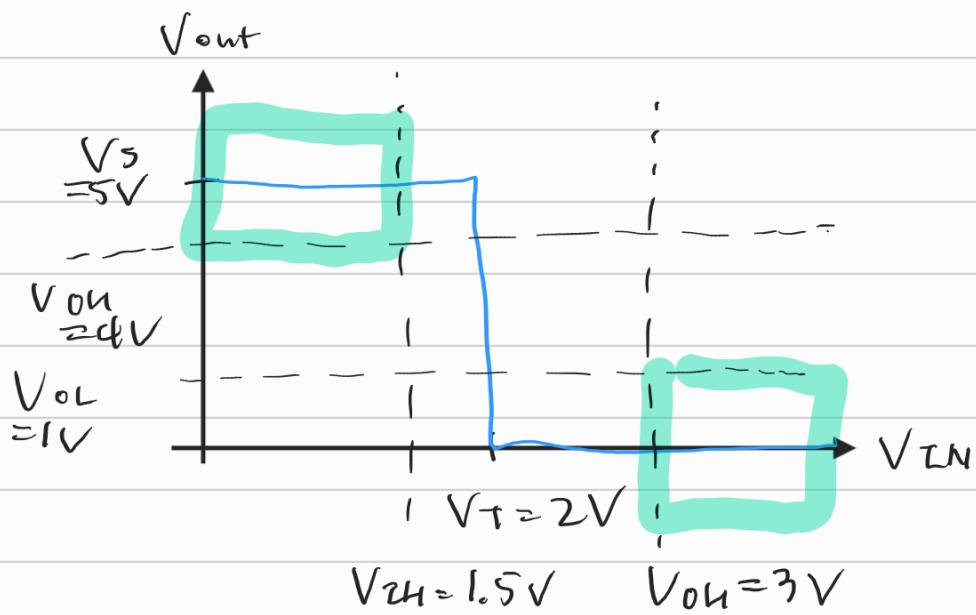
Therefore, the inverter satisfies the static discipline.



Previous exam (2019 1st exam)

4(a)

1) D<sub>1</sub> off, D<sub>2</sub> off

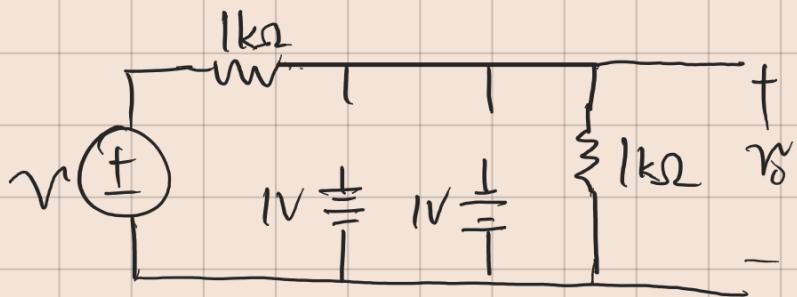


$$V_o = \frac{1}{2}V$$

For D<sub>1</sub> to be off,  $V_o - 1 < 0 \rightarrow V < 2$

For D<sub>2</sub> to be off,  $-1 - V_o < 0 \rightarrow V > -2$

$$\therefore V_o = \frac{1}{2}V, -2 < V < 2$$

2) D<sub>1</sub> on, D<sub>2</sub> off

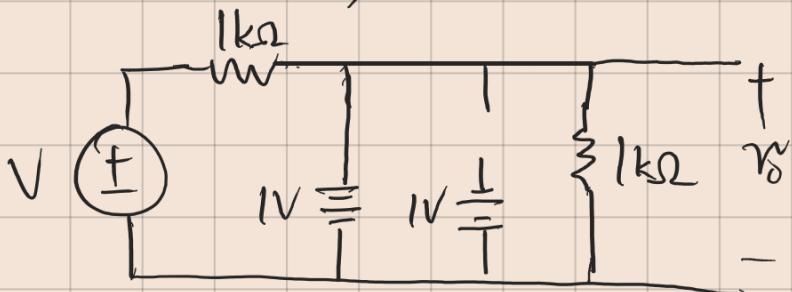

$$V_o = 1V$$


For D<sub>1</sub> to be on,  $(V - V_o) - 1 \geq 0$   
 $V \geq 2$

For D<sub>2</sub> to be off,  $-1 - V_o < 0$

always true ( $V_o = 1V$ )

$$\therefore V_o = 1, V \geq 2$$

3)  $D_1$  off,  $D_2$  on

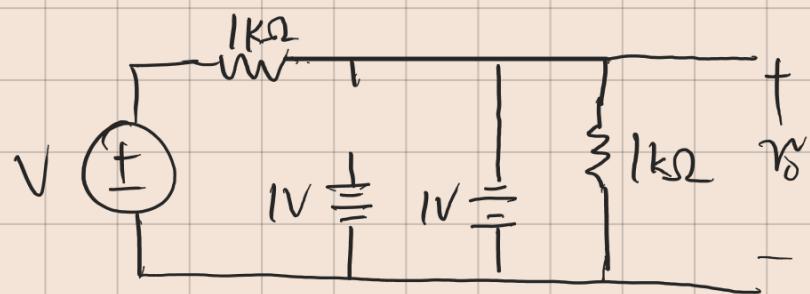

$$V_o = -1 \text{ V}$$

For  $D_1$  to be off,  $V_o - 1 < 0$

always true ( $V_o = -1 \text{ V}$ )

For  $D_2$  to be on,  $-1 - (V - V_o) \geq 0$

$$V \leq -2$$

$$\therefore V_o = -1, V \leq -2$$

4)  $D_1$  on,  $D_2$  on

For  $D_1$  to be on,  $V - V_o - 1 \geq 0$


$$V_o \leq V - 1$$

For  $D_2$  to be on,  $-1 - (V - V_o) \geq 0$

$$V_o \geq V + 1$$


$\nexists V$ , It is not possible.

Output waveform

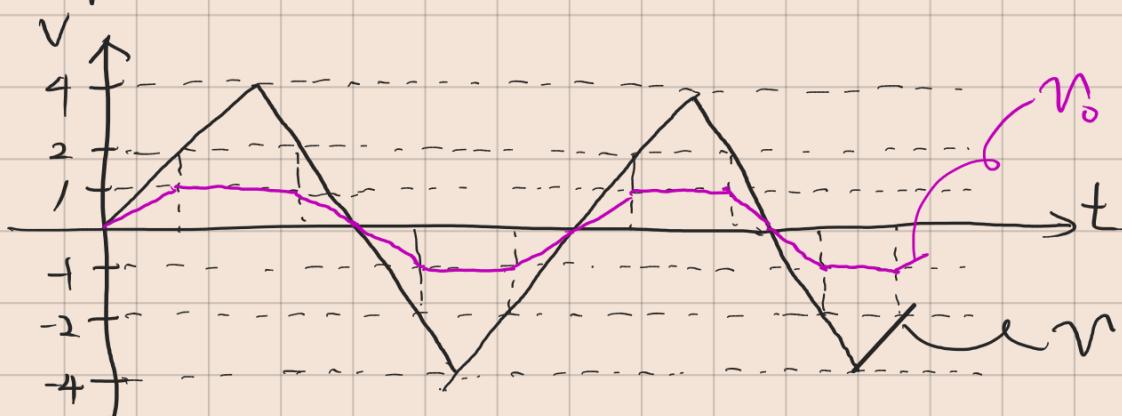

4(b)

1) D<sub>1</sub> off, D<sub>2</sub> off

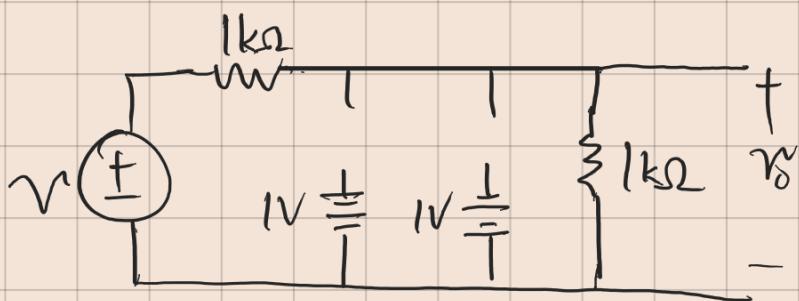


$$V_o = \frac{1}{2}V$$

For D<sub>1</sub> to be off,  $V_o - 1 < 0.6 \rightarrow V < 3.2$

For D<sub>2</sub> to be off,  $-1 - V_o < 0.6 \rightarrow V > -3.$

$$\therefore V_o = \frac{1}{2}V, -3.2 < V < 3.2$$

2) D<sub>1</sub> on, D<sub>2</sub> off

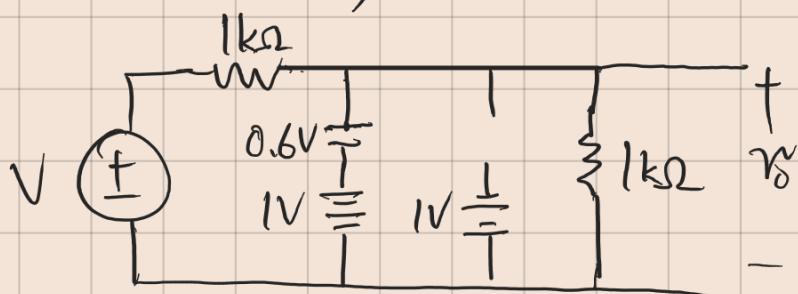

$$V_o = 1.6V$$

For D<sub>1</sub> to be on,  $(V - V_o) - 1 \geq 0.6$


$$V \geq 3.2$$

For D<sub>2</sub> to be off,  $-1 - V_o < 0.6$

always true ( $V_o = 1.6V$ )

$$\therefore V_o = 1.6, V \geq 3.2$$

3)  $D_1$  off,  $D_2$  on

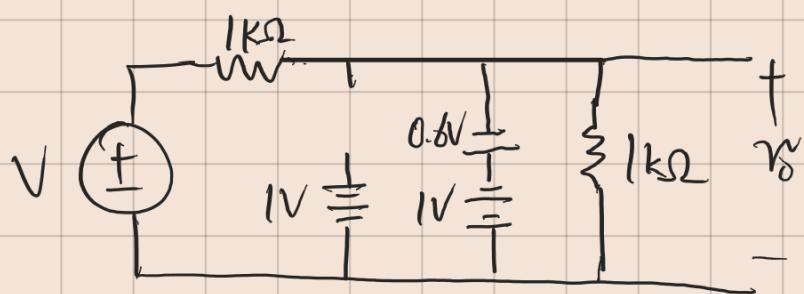

$$V_o = -1.6V$$

For  $D_1$  to be off  $V_o - 1 < 0.6$

always true ( $V_o = -1.6V$ )

For  $D_2$  to be on,  $-1 - (V - V_o) \geq 0.6$

$$V \leq -3.2$$

$$\therefore V_o = -1.6, V \leq -3.2$$

4)  $D_1$  on,  $D_2$  on

For  $D_1$  to be on,  $V - V_o - 1.6 \geq 0$

$$V_o \leq V - 1.6$$

For  $D_2$  to be on,  $-1.6 - (V - V_o) \geq 0$

$$V_o \geq V + 1.6$$

$\nexists V$ , It is not possible.

Output waveform

