

EEC HW5 2021-16988 Jaewan Park.

Exercise 12.2

(a)


$$V_s - \frac{V_1}{8} + \frac{V_1 - V_2}{6} + \frac{1}{24} \frac{dV_1}{dt} = 0$$

$$V_s - \frac{V_1 - V_2}{6} = \frac{1}{12} \frac{dV_2}{dt}$$


$$\Rightarrow \frac{d^2V_2}{dt^2} + 10 \frac{dV_2}{dt} + 9V_2 = 0$$

$$\Rightarrow V_2 = A_1 e^{-9t} + A_2 t e^{-9t}, \quad A_1 = -\frac{3}{8}, \quad A_2 = \frac{3}{8}$$

$$\therefore V_2(t) = -\frac{3}{8} e^{-9t} + \frac{3}{8} t e^{-9t}$$

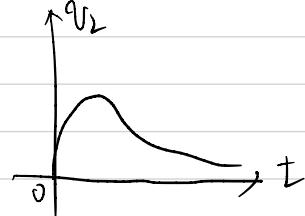

Problem 12.6

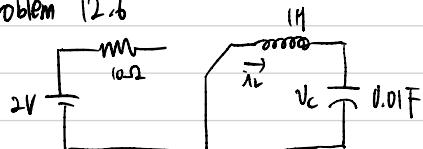


$$V_C(\omega) = j\omega C = 2, \quad i_R(\omega) = j\omega C = 0$$

$$\Rightarrow i_L = 0.01 \frac{dV_L}{dt}, \quad V_C + 1 \cdot \frac{dV_L}{dt} = 0$$

$$\therefore \frac{d^2i_L}{dt^2} + 100 i_L = 0, \quad i_L = A_1 e^{10jt} + A_2 e^{-10jt}$$

$$\Rightarrow A_1 = -0.1j, \quad A_2 = 0.1j$$

$$\therefore i_L(t) = -0.2 \sin 10t, \quad V_C(t) = 2 \cos 10t$$

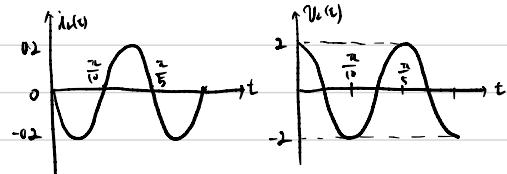

Exercise 13.13

(a) Using impedance,

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{j\omega R}}{R + \frac{1}{j\omega L} + \frac{1}{j\omega C}} = \frac{\frac{1}{j\omega R}}{1 + \frac{1}{20\pi R} + \frac{1}{20\pi C}} = \frac{1}{2 + 20\pi j\omega}$$

$$\therefore \text{Magnitude} = \frac{1}{\sqrt{4 + (20\pi\omega)^2}}$$

$$\text{phase} = \tan^{-1}(-10\omega)$$

$$(b) V_o(t) = \frac{1}{2\sqrt{1+100w^2}} \cos(\omega^2 n t + \phi) \quad (\tan \phi = -1/w)$$

Use superposition

$$① \cos(100t), w = 100 \times 10^{-3} = 0.1 \quad (w: rad/s)$$

$$\Rightarrow \phi = \tan^{-1}(-1) = -\frac{\pi}{4}, V_o(t) = \frac{1}{2\sqrt{2}} \cos(100t - \frac{\pi}{4})$$

$$② \cos(10000t), w = 10000 \times 10^{-3} = 10$$

$$\Rightarrow \phi = \tan^{-1}(-100), V_o(t) = \frac{1}{2\sqrt{1+10000}} \cos(10000t - \tan^{-1}(100))$$

$$\therefore V_o(t) = \frac{1}{2\sqrt{2}} \cos(100t - \frac{\pi}{4}) + \frac{1}{2\sqrt{1+10000}} \cos(10000t - \tan^{-1}(100))$$

Problem 13.4

$$(a) \frac{V_1}{V_o} = \frac{R_1 + j\omega L_1}{R + j\omega L + R_1 + j\omega L_1}$$

$$(b) DC: w=0$$

$$\therefore \frac{R_1}{R+R_1} = \frac{1}{10} \quad \therefore R = 9 \text{ k}\Omega$$

$$(c) \text{High Frequency: } w \rightarrow \infty$$

$$\therefore \frac{L_1}{L+L_1} = \frac{1}{10} \quad \therefore L = 90 \text{ mH}$$

Problem 15.12

① V_{TH}

$$\Rightarrow V_{TH} = R_1 \cdot jV_{TH}$$


$\Rightarrow V_{TH}$ should be 0

② R_{TH}

$$\Rightarrow i = jV + \frac{v}{R_1} = V \left(j + \frac{1}{R_1}\right)$$

$$\therefore R_{TH} = \frac{v}{i} = \frac{1}{j + \frac{1}{R_1}} = \frac{R_1}{1 + R_1 j}$$

Exercise 15.24

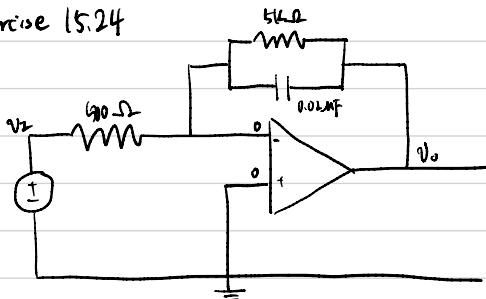


$$(a) \frac{V_2}{0.5} = \frac{0 - V_o}{5} + \frac{0 - V_o}{\frac{1}{j\omega \cdot 0.02}} = - \left(\frac{1}{5} + 10.2 \cdot \omega j \right) V_o$$

$$\therefore \frac{V_o}{V_2} = - \frac{5}{0.5 (1 + 10.2 \omega j)}$$

$$\omega = 0 \rightarrow \frac{V_o}{V_2} = -10$$

$$(b) \frac{V_o}{V_2} = - \frac{10}{1 + 10.2 \omega j}$$

Problem 15.34

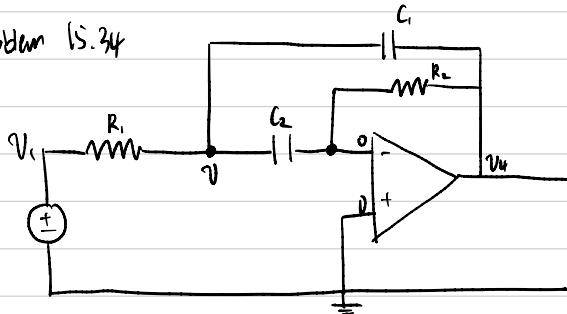

$$(a) \frac{V_1 - V}{R_1} = \frac{V - V_o}{j\omega C_1} + \frac{V}{j\omega C_2}$$

$$\frac{V}{j\omega C_2} = \frac{-V_o}{R_2}$$

$$\Rightarrow \frac{V_o}{V_1} = - \frac{1}{\frac{R_1(C_1+C_2)}{R_2C_2} + j \left(R_1C_1W - \frac{1}{\omega R_2 C_2} \right)}$$

$$(c) \left| \frac{V_4}{V_1} \right| = \frac{1}{\sqrt{\left(\frac{R_1(C_1(s))}{R_2 C_2} \right)^2 + \left(\omega R_1 - \frac{1}{\omega R_2 C_2} \right)^2}}$$


$$\omega \rightarrow 0 : \left| \frac{V_4}{V_1} \right| \rightarrow 0, \quad \omega \rightarrow \infty : \left| \frac{V_4}{V_1} \right| \rightarrow 0 \quad \therefore \text{Band Pass Filter.}$$

∴ Bandwidth

$$\Rightarrow \omega R_1 C_1 - \frac{1}{\omega R_2 C_2} = \pm \frac{R_1(C_1(s))}{R_2 C_2}$$

$$\omega^2 \pm \frac{C_1 C_2}{R_2 C_1 C_2} \omega - \frac{1}{R_1 R_2 C_1 C_2} = 0$$

$$\Rightarrow \therefore |(\omega_2 - \omega_1)| = \frac{C_1 C_2}{R_2 C_1 C_2}$$

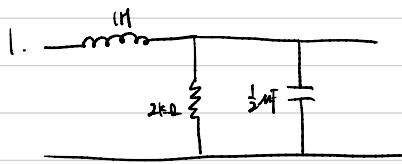

$$(a) Z(j\omega) = j\omega + 2 // \frac{1}{j\omega} \\ = \frac{2}{1+j\omega} + \left(\omega - \frac{2\omega}{1+j\omega} \right) j$$



$$\therefore \omega = \frac{2\omega}{1+j\omega} \Rightarrow \omega = 1$$

$$(b) H(j\omega) = \frac{2 // \frac{1}{j\omega}}{Z(j\omega)} = \frac{2}{(2-\omega^2) j\omega}$$

$$\therefore |H(j\omega)| = \frac{2}{\sqrt{(2-\omega^2)^2 + \omega^2}}$$

$$\omega \rightarrow 0 : |H(j\omega)| \rightarrow 1 \quad \max: \omega = \frac{\sqrt{3}}{2}, \quad |H(j\omega)| = \frac{4}{\sqrt{7}}$$

$$\omega \rightarrow \infty : |H(j\omega)| \rightarrow 0$$

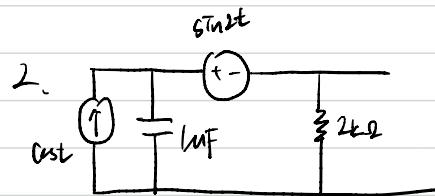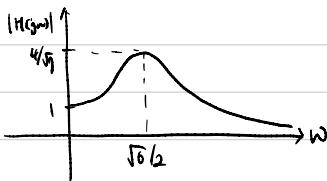

Use Superposition

$$① \text{Cst} \leftarrow e^{j\omega t} \quad (\omega=1)$$

$$|H(j\omega)| = \left(\frac{1}{j} // 2 \right) \cdot 1 = \frac{2}{1+j\omega}$$

$$\therefore V_o(t) = \frac{2}{\sqrt{3}} \cos(t - \theta_1) \cdot \tan \theta_1 \cdot 2$$

$$② \text{Sin} \omega t \leftarrow -j \cdot e^{j\omega t} \quad (\omega=2)$$

$$|H(j\omega)| = \frac{2}{2 + \frac{1}{2j}} \cdot j = \frac{4}{-1 - 4j}$$

$$\therefore V_o(t) = \frac{4}{\sqrt{15}} \cos(2t - \theta_2), \quad \tan \theta_2 = 4$$

$$\therefore V_o(t) = \frac{2}{\sqrt{3}} \cos(t - \theta_1) + \frac{4}{\sqrt{15}} \cos(2t - \theta_2)$$