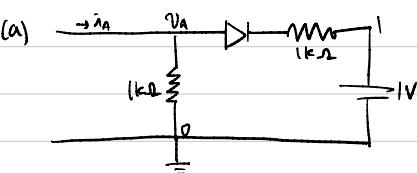


EEC HW2 : 2021-16988 Jaewan Park.

Exercise 4.4




i) Diode off: $V_A < 1$


$$i_A = \frac{V_A}{1 \text{ k}\Omega} = V_A$$

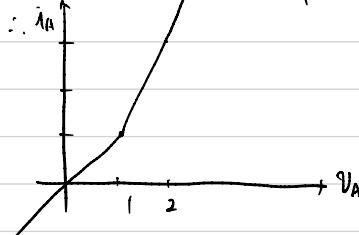ii) Diode on: $V_A \geq 1$

Node analysis: $i_A = \frac{V_A - 0}{1} + \frac{V_A - 1}{1} = 2V_A - 1$




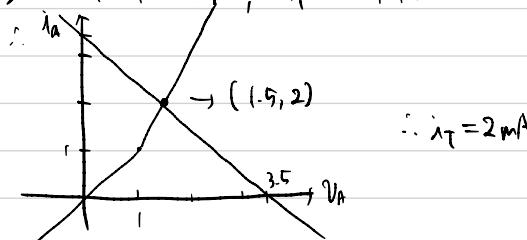(b) $3.5 = 1(i_A + V_T), i_A = -V_T + 3.5$



$$\therefore i_A = 2 \text{ mA}$$

Problem 4.4

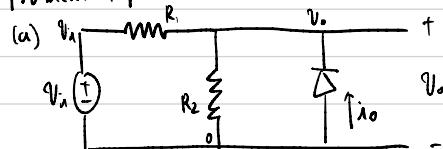


i) Diode off: $i_A = 0, V_o > 0$

$$V_o = V_{A1} \times \frac{R_2}{R_1 + R_2} = \frac{1}{2} V_A > 0. \quad \therefore V_A > 0$$

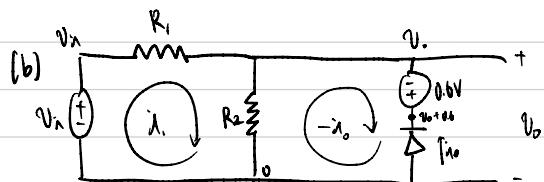ii) Diode on: $V_o = 0, i_A \geq 0$

$$i_A = -\frac{V_A}{R_1} \geq 0, \quad \therefore V_A \leq 0$$

$$\therefore V_o = \begin{cases} \frac{1}{2} V_A & (V_A > 0) \\ 0 & (V_A \leq 0) \end{cases}$$



i) Diode off: $i_A = 0, V_o + 0.6 > 0$

$$V_o = \frac{1}{2} V_A > -0.6, \quad \therefore V_A > -1.2V$$

ii) Diode on: $V_o + 0.6 = 0, i_A \geq 0$

Loop analysis: $V_A = R_1 i_A + R_2 (i_1 + i_o)$

$$0.6 = R_2 (-i_o - i_1)$$

$$i_1 = \frac{V_A + 0.6}{R_1}, \quad i_o = -\frac{V_A + 1.2}{R_1} \geq 0$$

$$\therefore V_A \leq -1.2V$$

$$\therefore V_o = \begin{cases} \frac{1}{2} V_A & (V_A > -1.2V) \\ 0.6V & (V_A \leq -1.2V) \end{cases}$$

Problem 4.13

$$V_A = 10^{-3} \sin(\omega t), \quad V_N = 10, \quad \lambda_N = 10^{-4} V_N^2 = 10^{-2}$$


$$\lambda_N = I_N + i_n = 10^{-4} V_N^2 = 10^{-4} V_N^2 + 2 \cdot 10^{-4} V_N \cdot v_n$$

$$i_n = 2 \cdot 10^{-4} V_N \cdot v_n$$

$$r_N = \frac{1}{2 \cdot 10^{-4} V_N} = 500$$

$$v_{out} = v_n \times \frac{R}{r_N + R} = \frac{R}{R+500} 10^{-3} \sin(\omega t)$$

Exercise 5.8

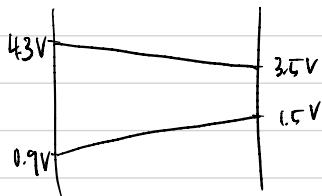

(a) Output: $0.9V < v < 4.3V$, Input: $1.5V < v < 3.5V$

will be treated invalid

$$(b) NM_H = 4.3V - 3.5V = 0.8V$$

$$NM_L = 1.5V - 0.9V = 0.6V$$

Problem 5.10

$$0 < V_{ZN} < V_{IL} \Rightarrow V_{on} < V_{out} < 5$$



$$V_{IL} < V_{ZN} < 5 \Rightarrow 0 < V_{on} < V_{IL}$$

∴ C.

Problem 6.3


$$(a) V_{IN} < V_T \Rightarrow V_{out} > V_S$$

$$V_{IN} > V_T \Rightarrow V_{out} = 0$$

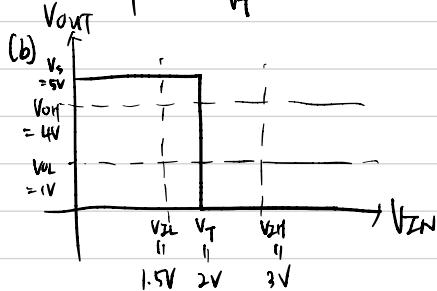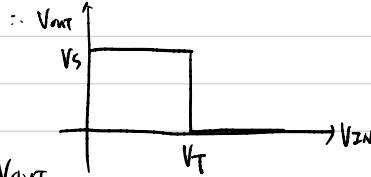

\therefore Yes

2019 1st exam - H.

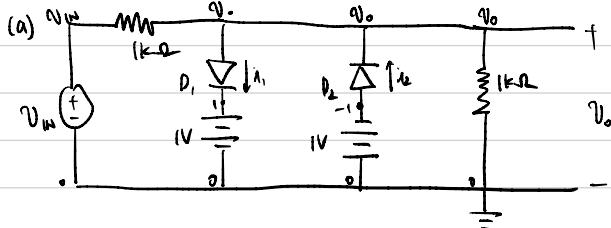

$$\text{i)} D_1 \text{ off, } D_2 \text{ off : } i_1=0, i_2=0, V_o < 0, -1 - V_o < 0 \Rightarrow -1 < V_o < 1, i_1=0, i_2=0$$


$$V_o = V_{IN} \times \frac{1}{1+1} = \frac{1}{2} V_{IN}, -1 < \frac{1}{2} V_{IN} < 1, \therefore -2 < V_{IN} < 2$$


$$\text{ii)} D_1 \text{ off, } D_2 \text{ on : } i_1=0, V_o < 0, V_o = -1, i_2 \geq 0 \Rightarrow V_o = -1, i_1=0, i_2 \geq 0$$

$$i_2 = -\frac{V_{IN}}{1} - \frac{1}{1+1} = -V_{IN} - 2 \geq 0, \therefore V_{IN} \leq -2 \quad (\because \text{superposition})$$

$$\text{iii)} D_1 \text{ on, } D_2 \text{ off : } V_o = 1, i_1 \geq 0, i_2 = 0, -1 - V_o < 0 \Rightarrow V_o = 1, i_1 \geq 0, i_2 = 0$$
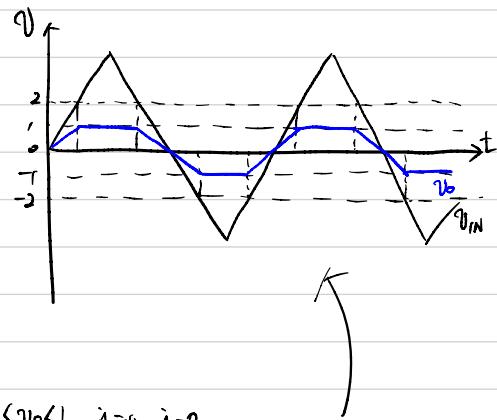
$$i_1 = \frac{V_{IN}}{1} - \frac{1}{1+1} = V_{IN} - 2 \geq 0, \therefore V_{IN} \geq 2 \quad (\because \text{superposition})$$



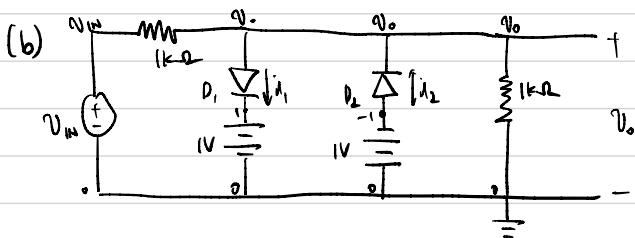

i) D₁ off, D₂ off $\Rightarrow i_1 = 0, V_o > 0.6, i_2 = 0, -V_o < 0.6 \Rightarrow -1.6 < V_o < 1.6, i_1 = 0, i_2 = 0$

$$V_o = \frac{1}{2} V_{IN}, -1.6 < \frac{1}{2} V_{IN} < 1.6, -3.2 < V_{IN} < 3.2$$

ii) D₁ off, D₂ on $\Rightarrow i_1 = 0, V_o > 0.6, -V_o = 0.6, i_2 \geq 0 \Rightarrow V_o = -1.6, i_1 = 0, i_2 \geq 0$

$$i_2 = -\frac{V_o}{1/1} = -V_{IN} - 3.2 \geq 0, V_{IN} \leq -3.2 \quad (\because \text{superposition})$$

iii) D₁ on, D₂ off $\Rightarrow V_o > 0.6, i_1 \geq 0, i_2 = 0, -V_o < 0.6 \Rightarrow V_o = 1.6, i_1 \geq 0, i_2 = 0$

$$i_1 = \frac{V_o}{1/1} = V_{IN} - 3.2 \geq 0, V_{IN} \geq 3.2 \quad (\because \text{superposition})$$

$$\therefore V_o = \begin{cases} \frac{1}{2} V_{IN} & (-3.2 < V_{IN} < 3.2) \\ -1.6 & (V_{IN} \leq -3.2) \\ 1.6 & (V_{IN} \geq 3.2) \end{cases}$$

