

EEC HW4 2021-16988 Jaewan Park

Exercise 10.11


$$R_{TH} = R_1 // R_2 = \frac{2}{3} \text{ k}\Omega$$

$$V_{TH} = V_S \times \frac{R_2}{R_1 + R_2} = \begin{cases} 0V & (t < 0) \\ 2V & (t > 0) \end{cases}$$

$$\Rightarrow V_C(0) = 0V, V_C(\infty) = 2V$$


$$\therefore V_C(t) = 2 + (0 - 2)e^{-t/\tau} \quad (\tau = R_{TH}C = \frac{20}{3} \text{ ms})$$

$$= 2 - 2e^{-\frac{3}{20}t}$$

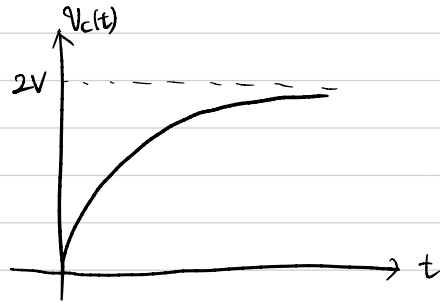

Problem 10.1

(a)

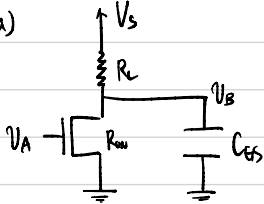

① Rise Time

$$V_B(0^-) = V_S \cdot \frac{R_{TH}}{R_L + R_{TH}} = V_B(0^+) \quad (\because \text{continuous}), \quad V_B(\infty) = V_S$$

$$\therefore V_B(t) = V_S + \left(V_S \cdot \frac{R_{TH}}{R_L + R_{TH}} - V_S \right) e^{-t/\tau_r} \quad (\tau_r = R_L C_{TH})$$

$$= V_S - V_S \cdot \frac{R_L}{R_L + R_{TH}} e^{-t/\tau_r}$$

$$V_B(t_r) = V_H \Rightarrow t_r = R_L C_{TH} \ln \frac{V_S R_L}{(V_S - V_H)(R_L + R_{TH})}$$

② Fall Time.

$$V_B(0^-) = V_S = V_B(0^+), \quad V_B(\infty) = V_S \cdot \frac{R_{TH}}{R_L + R_{TH}}$$

$$\therefore V_B(t) = V_S \cdot \frac{R_{TH}}{R_L + R_{TH}} + \left(V_S - V_S \cdot \frac{R_{TH}}{R_L + R_{TH}} \right) e^{-t/\tau_f} \quad (\tau_f = R_{TH} C_{TH} = \frac{R_L R_{TH} C_{TH}}{R_L + R_{TH}})$$

$$= V_S \cdot \frac{R_{TH}}{R_L + R_{TH}} + V_S \cdot \frac{R_L}{R_L + R_{TH}} e^{-t/\tau_f}$$

$$V_B(t_f) = V_L \Rightarrow t_f = \frac{R_L R_{TH} C_{TH}}{R_L + R_{TH}} \ln \frac{V_S R_L}{V_L (R_L + R_{TH}) - V_S R_{TH}}$$

(b) $t_r \approx 8.2 \text{ ns}$, $t_f \approx 1.9 \text{ ns}$

\therefore propagation delay = 8.2 ns


Problem 10.12

$$0 \leq t \leq t_1: V_O(t) = V_S + (V_{min} - V_S) e^{-t/\tau_C}$$

$$t_1 \leq t \leq t_1 + t_2: V_O(t) = 0 + (V_{max} - 0) e^{-(t-t_1)/\tau_C}$$


Average voltage: $V_S = \frac{V}{2} + (\text{square wave between } \frac{V}{2}, -\frac{V}{2})$

$$\Rightarrow \text{Average } V_O = \frac{V}{2}$$

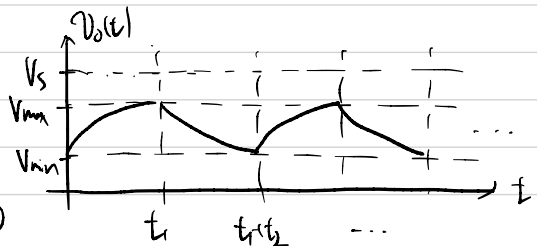

Exercise 11.1

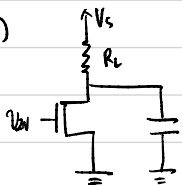(a) When $V_{IN} = 0$, $P_{steady-state} = 0$



(b) When $V_{IN} = 1$, $P_{steady-state} = V_S \cdot i_0 = V_S \cdot \frac{V_S}{R_L + R_{ON}} = \frac{V_S^2}{R_L + R_{ON}}$

(c) $P_{static} = \frac{V_S^2}{2(R_L + R_{ON})}$

$$P_{dynamic} = C_L f \cdot \left(\frac{R_L V_S}{R_L + R_{ON}} \right)^2 = \frac{C_L}{2T} \cdot \left(\frac{R_L V_S}{R_L + R_{ON}} \right)^2$$

(d) (i) $\times \frac{1}{2}$

(ii) $\times \frac{1}{4}$

(iii) $\times \frac{1}{2}$

(e) For $V_{OL}^+ \leq V_{OL}$, $V_S \cdot \frac{R_{ON}}{R_L + R_{ON}} \leq V_{OL}$, $R_L \geq R_{ON} \left(\frac{V_S}{V_{OL}} - 1 \right)$

$\bar{P} = P_{static} + P_{dynamic}$, and $P_{static} \gg P_{dynamic}$, so

$R_L \uparrow \Leftrightarrow \bar{P} \downarrow$.

\therefore We should increase R_L as much as possible, satisfying the static discipline


No upper limit exists, $\therefore R_L = \infty$

Problem 11.1

(a) The truth table is as the following. ($Z = A \bar{B}$)

A	B	Z
0	0	0
0	1	0
1	0	1
1	1	0

\Rightarrow

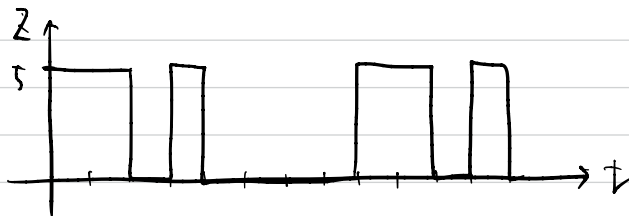

$$(b) P_{\text{static}} = \begin{cases} \frac{V_i^2}{R_L} & (0 \leq t \leq T_1) \\ \frac{2V_s^2}{R_L} & (T_1 \leq t \leq T_2) \\ \frac{V_s^2}{R_L} & (T_2 \leq t \leq T_3) \\ \frac{V_s^2}{R_L} & (T_3 \leq t \leq T_4) \end{cases}$$

$$\therefore \overline{P_{\text{static}}} = \frac{T_1}{T_4} \cdot \frac{V_s^2}{R_L} + \frac{T_2 - T_1}{T_4} \cdot \frac{2V_s^2}{R_L} + \frac{T_3 - T_2}{T_4} \cdot \frac{V_s^2}{R_L} + \frac{T_4 - T_3}{T_4} \cdot \frac{V_s^2}{R_L}$$

$$= \frac{T_1 + T_2 - T_1}{T_4} \cdot \frac{V_s^2}{R_L}$$

(c) $C_G, C_L \Rightarrow$ over. twice charge & discharge each


$$\therefore \overline{P_{\text{dynamic}}} = \frac{C_G V_s^2}{T_4} + \frac{2C_L V_s^2}{T_4}$$

$$= \frac{(C_G + 2C_L) V_s^2}{T_4}$$

(d) $\overline{P_{\text{static}}} = 2.9 \text{ mW}$

$\overline{P_{\text{dynamic}}} = 87.5 \text{ mW}$

(c)

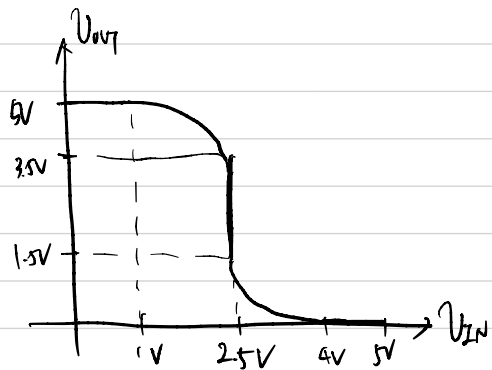

Previous Exam

(a) $P_{\text{dynamic}} = C \cdot \frac{f}{2} \cdot V_D^2 = 1.25 \text{ W}$

(b). Both saturated

$$\Rightarrow I_{DN} = I_{DP}, \quad 0.1(V_{2N} - 1)^2 = 0.1(5 - V_{2N})^2$$

$$\therefore V_{2N} = 2.5 \text{ V}$$

For saturation, we have

$$V_{2N} \geq V_{TN}, \quad V_{2N} - V_{OUT} < V_{TN}, \quad V_{2N} - 5 \leq V_{TP}, \quad V_{2N} - V_{OUT} > V_{TP}$$

$$\therefore 1.5 \text{ V} < V_{OUT} < 3.5 \text{ V} \quad (\text{when } V_{2N} = 2.5 \text{ V})$$